

## Application Note 5302

### Introduction

A Solid State Relay (SSR) is a solid state replacement of the electromechanical relays (EMR), and has been used for general purpose switching of signals and AC/DC loads. A SSR provides both switching and galvanic isolation functions without any mechanical movement during its operation. A SSR consists of the light emitting diode (LED), photodiode array, MOSFET drivers and the high-voltage MOSFETs. The LED on the input control side converts the electrical input signal into the optical signal. On the output side, the optical signal is converted back to the electrical signal that supplies the power to switch the MOSFETs. The purpose of this application note is to describe the input control drive circuits for the LED, the various loads of the SSR and the surge characteristics of Avago Technologies' new SSR product family, the ASSR series.

### Input Control Drive Circuits

Operation of the ASSR Series requires at least 3 mA of input current. Higher input current drive results in faster switching time of the ASSR, though the turn-off time,  $T_{OFF}$ , does not reduce as much as turn-on time,  $T_{ON}$ ;  $T_{OFF}$  is usually much shorter than  $T_{ON}$ . A simple circuit for obtaining the desired input forward current,  $I_F$ , and input OFF voltage,  $V_{F(OFF)}$ , is shown in Figure 1.

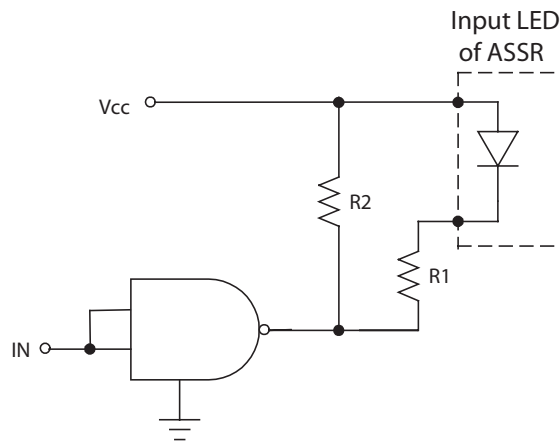


Figure 1. Logic-Driven Control Circuit.

The logic series used can be almost anything; any device from the TTL logic family, open-collector or totem pole, will work in the arrangement shown. The same is true for CMOS, provided only that the current-sinking capability is adequate. Current limiting resistor  $R_1$  sets  $I_F$ , and it can be calculated by

$$R_1 = (V_{CC} - V_{OL} - V_F) / I_F$$

where  $V_{OL}$  is the low level output voltage of the gate, and  $V_F$  is the forward voltage of the LED.  $V_{CC}$  is the supply

The purpose of resistor  $R_2$  is to bypass logic-high leakage current with sufficiently small voltage drop to ensure a  $V_{F(OFF)}$  less than 0.8 V. With open-collector TTL outputs,  $R_2$  is always required. And it should meet

$$R_2 < V_{F(OFF)} / I_{OH}$$

where  $I_{OH}$  is the high level output current.

$R_2$  is not required if the logic output has an internal pull-up circuit that is able to satisfy the  $V_{F(OFF)}$  requirement of the ASSR.

The circuit in Figure 1 is basically a series-drive type because the active current is switched by a device in series with the LED. This type of drive circuit has a great deal of flexibility in achieving other design objectives. It can be used with TTL having either an active pull-up (totem-pole) output or open-collector output.

If an open collector TTL is available for driving the input control, a simpler alternative is the shunt-driven circuit as shown in Figure 2.

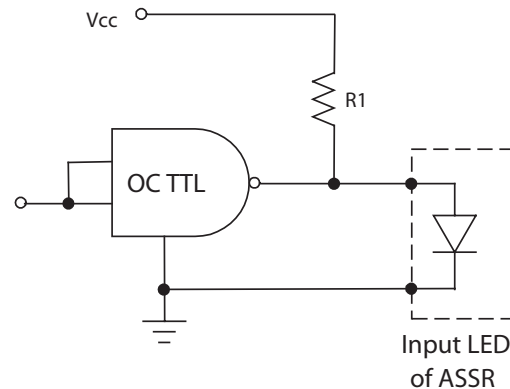


Figure 2. Shunt-Driven Control Circuit

It requires only a single resistor,  $R_1$ , and the logic-low voltage does not influence the  $I_F$ . The LED is switched off by directing current away from it with the shunt output transistor within the gate. When the output of the logic gate goes low, current is shunted away from the LED, and the ASSR turns off. Thus, the  $V_{F(OFF)}$  requirement is inherently satisfied by the logic-low voltage. When the logic-gate output goes high,  $I_F$  is limited by the current limiting resistor  $R_1$ , which is calculated by

$$R_1 = (V_{CC} - V_F) / I_F$$

For the open collector gates, this configuration eliminates the extra pull-up resistor,  $R_2$ , required by the series-drive type shown in Figure 1.

The switching time is influenced by the level of input forward current,  $I_F$ . As it increases,  $T_{ON}$  becomes shorter. It may not be desirable to operate with a high  $I_F$  as it would increase the output offset voltage,  $V_{(OS)}$ , due to heat transferred from the LED control to the MOSFETs at the output. Consequently, when the ASSR is used in measuring instruments, a high  $V_{(OS)}$  would inevitably give an error in measurement. A high  $I_F$  also increases the input power consumption and accelerates LED's light output power (LOP) degradation. It is cautioned that the input power should not exceed the input power dissipation value,  $P_{IN}$ , as stated in the absolute maximum ratings in the datasheet. The LOP degradation is a function of temperature, time, and  $I_F$ . In general, LOP degradation occurs up to about 1000 hours, at which point the degradation stabilizes.

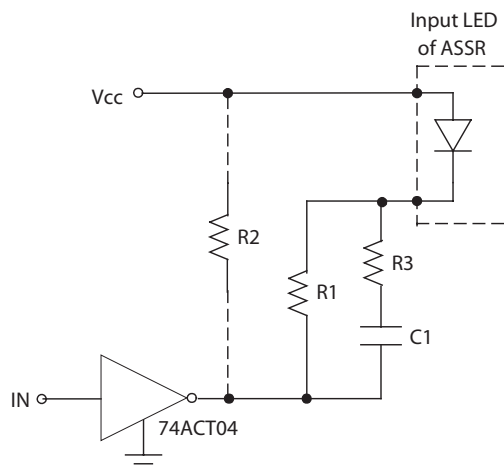


Figure 3. Recommended Peaking Control Circuit

In situations requiring fast  $T_{ON}$  but low  $V_{(OS)}$ , a peaking circuit, consisting of resistor  $R_3$  and capacitor  $C_1$ , shown in figure 3 can be considered. When the logic output is high,  $R_2$  ensures that the current through the LED is so small that  $C_1$  is completely discharged. When the logic output goes low, a surge of current flows through both  $R_1$  and  $R_3$  until  $C_1$  is charged to the voltage across  $R_1$ . For the ASSR Series,  $C_1$  is recommended to be  $10\mu F$ .

Table 1. Typical Peaked Turn-on Time with  $C_1 = 10\mu F$

$R_3 (\Omega)$	$I_{cc}(mA)$	$T_{on} (ms)$
-	10	0.15
680	11	0.10
330	11	0.08
33	12	0.015

Table 1 illustrates the influence of the peaking circuit on the  $T_{ON}$  of the ASSR-3220 (250 V, 0.2 A,  $10\Omega$ ) where  $T_{ON}$  includes the propagation delay time. Thus the peaking circuit permits fast  $T_{ON}$  as well as low  $I_F$ . Switching on the output MOSFETs requires charging the gate capacitances in the MOSFET driver circuit. This charge is the time-integrated photocurrent from the photodiode array and translates into a certain amount of current that must pass through the LED. The corresponding amount of LED charge is set by the value of the peaking capacitor,  $C_1$ , and the voltage across  $R_1$ . For this reason, it is not necessary to change the value of  $C_1$  when other values of peak current are desired; it is necessary only to change the value of  $R_3$  and make sure that the logic output is capable of sinking the higher current.

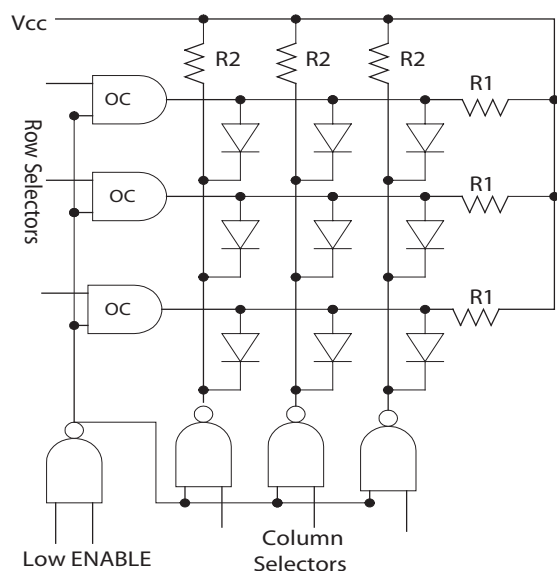
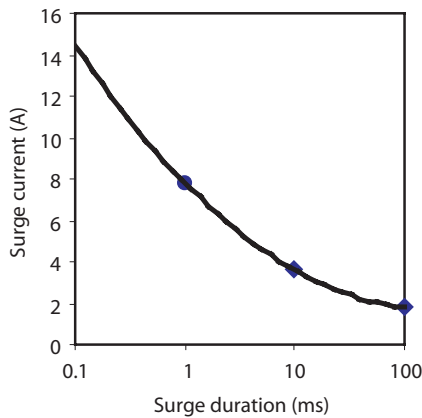


Figure 4. Matrix-Driven Control Circuit

Figure 4 shows a combination of series-shunt drive. The column drivers do the series switching and the row drivers operate in shunt mode. With the ENABLE input high, selection is made of the desired row and column (high true), but the selected LED remains OFF until the ENABLE goes low. This provision is necessary to ensure "break-before-make" operation of the output contacts. With turn-off time longer than turn-on time, there must be a "dead" time of 0.2 msec or more to prevent overlapping contact closure. The values of resistor  $R_1$  and  $R_2$  are selected as described for the circuits of figures 1 and 2, and, if desired, the peaking circuit consisting of  $R_3$  and  $C_1$  may be added in parallel with each  $R_1$ .

The matrix arrangement in Figure 4 is worth considering only if a very large number of switches are to be selectively operated. To make a selection from a smaller number of switches, a much simpler circuit is shown in Figure 5, where a decoder or de-multiplexer IC is used.

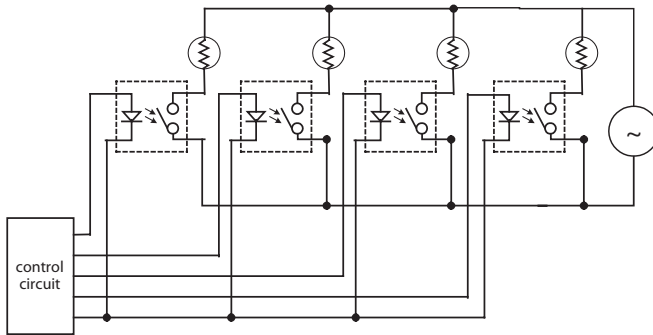




**Figure 6. ASSR-3220 Peak Surge Current as a Function of the Surge Current Duration at 25°C**

Figure 7 illustrates the use of SSRs in a lamp sequence control. Some areas that use SSRs to control lamp loads include process equipment, navigational devices, illuminated signs, and games. In aircraft applications, SSRs may control lamps for cabin lighting, instrumentation lighting, and status indicators. Ten units of the ASSR3220 were tested at room temperature under these conditions:

Input current,  $I_F=10$  mA (1Hz), lamp bulb as load, and load voltage,  $V=230$  VAC, 60 Hz. Each unit was tested for 1 million cycles. All units passed without catastrophic failure.



**Figure 7. Lamp Control**


Compared to EMRs, SSRs are especially useful in aircraft environments because they are immune to shock and vibration and are unaffected by electro-magnetic interference. Upon turn-on, the current through a lamp is very high initially because of the Tungsten filament's low resistance at room temperature. The current decreases as the filament heats up. Hence, the inrush current can be reduced by using a "keep alive" voltage across the filament to keep it warm but below the level of incandescence.

Similar to a lamp load, a capacitive load will cause a surge current to flow through the output MOSFETs of the SSR upon initial turn-on. This surge current will depend on the load capacitor value and the rate of rise of the load voltage. In addition, the frequency at which the SSR is switched will affect the output power dissipation.

Ten units of the ASSR-3220 were tested at room temperature under these conditions:

Input current,  $I_F=10$  mA (1Hz), 100  $\mu$ F capacitor as load, and load voltage  $V=230$  VAC, 60 Hz. The capacitor is charged by the load voltage through a 1.25 k $\Omega$  series resistor. The ASSR is parallel with the capacitor to discharge it when the ASSR is on. Each unit was tested for 1 million cycles. All units passed without catastrophic failures.

The ASSR-3220 can be used to drive fractional horsepower motors. A reversing control for a synchronous AC motor is shown in Figure 8. For motors that cycle on and off frequently, a SSR is often preferred over an EMR because it can handle surges better and does not produce EMI. A SSR might also be used to control small DC motor loads such as computer disk drives, VCD, DVD drives, various audio or video drives, household electronic appliances or automotives electronics. A SSR can also used to control the input coil of an EMR, which is an inductive load. Other inductive loads include small transformers, contactors, solenoid valves, etc. When a SSR drives an inductive loads, very high transient voltage can occur across the output of the SSR when it is turned off. The ASSR3220 can withstand a reasonable amount of inductive overload.

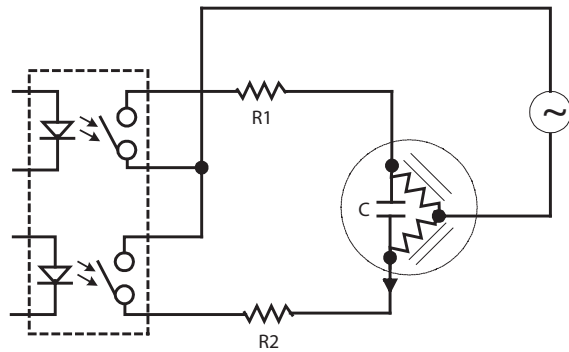

**Figure 8. Motor Reversing Control**

Ten units of the ASSR3220 were tested at room temperature under these conditions:

Input current,  $I_F=10$  mA (1Hz), 8 mH inductor as load, load voltage  $V=230$  VAC, 60 Hz, and load current is 0.2 A. Each unit was tested for 1 million cycles. All passed without catastrophic failures.

## Overvoltage Protection

In some applications, there is a possibility that the contacts may be exposed to destructively high voltages. For example, lightning can introduce high voltage surge into the telecommunication system. Over-voltage protection is always needed to protect an SSR. One such situation is partially illustrated in Figure 9, where the ASSR-3220 is being used to control the on/off-hook in a telephone set.

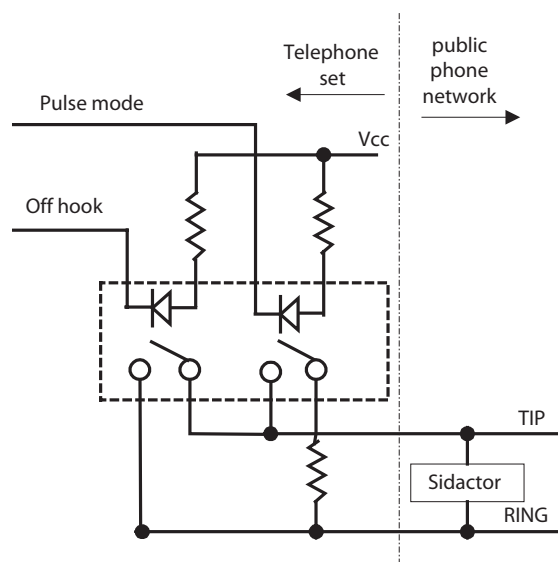


Figure 9. Protection Circuit for a Pulse Dialing Phone Set

When open, the contacts of the ASSR-3220 can withstand 250 V, positive or negative. Protection against damage due to exceeding 250 V is provided by the breakdown devices shown. These devices may be either General Semiconductor Sidactor, Trisil or MOV (Metal Oxide Varistors). They break down and conduct heavily when the voltage across them rises above a design level. As indicated by the symbol, the breakdown voltage is of either polarity, but single-polarity devices are also available. All of them fail "short" so protection does not fail even if operation does. The series resistors must be large enough to limit surge current to values specified for the protection devices. Selection of the breakdown voltage of the protection devices may depend on the particular situation.

For product information and a complete list of distributors, please go to our web site: [www.avagotech.com](http://www.avagotech.com)

Avago, Avago Technologies, and the A logo are trademarks of Avago Technologies in the United States and other countries. Data subject to change. Copyright © 2005-2010 Avago Technologies. All rights reserved. AV01-0527EN - July 15, 2010

**AVAGO**  
TECHNOLOGIES