

# Overview of High Performance Analog Optocouplers



## Application Note 1357

### Designing Analog Circuits Using the HCNR201

Internally, the HCNR201 analog optocoupler consists of two photo detectors symmetrically placed between the input LED. Thus, the radiant flux received by each of the two photodetectors is essentially the same, and forms the basis for the input-output linear transfer response. Unlike most other optocouplers, where the LED at the input is directly controlled, for the HCNR201 the input photodetector is generally placed in a servo feedback loop to control the LED current through the use of an external op-amp. This feedback loop has the most advantageous effect of compensating for any temperature related light output drift characteristics or other nonlinearities or aging effects of the LED.

Figure 1 shows the basic topology using the HCNR201 in the servo feedback loop. The HCNR201 is connected in a photovoltaic mode, as the voltage across the photodiodes is essentially zero volt. For a photoconductive operation the photodiodes are reverse biased as shown in Figure 2.

The two op-amps shown are two separate LM158 packages, and not two channels in a single dual package, otherwise galvanic insulation is not present as the grounds and Vcc are shared between the two op-amps of the dual package. The op-amp always tries to maintain the same voltage at its two inputs in a linear feedback, closed loop connection. Thus, the input side op-amp always tries to place zero volts across the photodiode 1 (PD1). As noted

before, in the photovoltaic mode of operation, the photodiode has either a forward bias or no bias applied across it. Thus, when  $V_{in}=0V$ , there is no photodiode 1 current ( $I_{PD1}$ ) and  $I_{PD2}$  is also zero. This is because  $I_{PD2} = K_3 \times I_{PD1}$  by the transfer gain  $K_3$  indicated in the data sheet ( $K_3 = I_{PD2} / I_{PD1} = 1$ ). Now, if some positive polarity voltage is applied at the input, the op-amp output would tend to swing to the negative rail (in this case the ground voltage) causing the LED current to flow. Then  $I_{PD1}$  is now externally set by  $V_{IN}$  and  $R_1$  ( $I_{PD1} = V_{IN}/R_1$ ). The op-amp will limit the LED current  $I_F$  to an appropriate value required to establish the externally set  $I_{PD1}$ . The maximum full scale LED current is designed to keep it under the absolute maximum rating of 25 mA. Since, the op-amp is connected in a stable negative feedback servo loop it also maintains the same voltages across its two inputs, in this case zero volts. The output voltage is just  $I_{PD2} \times R_2$ . Thus, to establish the transfer function the following equations can be written:

$$I_{PD1} = V_{IN}/R_1 \text{ (input photodiode current)}$$

$$K_3 = I_{PD2}/I_{PD1} = 1 \text{ (transfer gain indicated in the data sheet)}$$

$$I_{PD2} = K_3 \times I_{PD1}$$

$$V_{OUT} = I_{PD2} \times R_2$$

Solving the above equations readily yields the linear transfer function as  $V_{OUT}/V_{IN} = K_3 \times R_2/R_1$

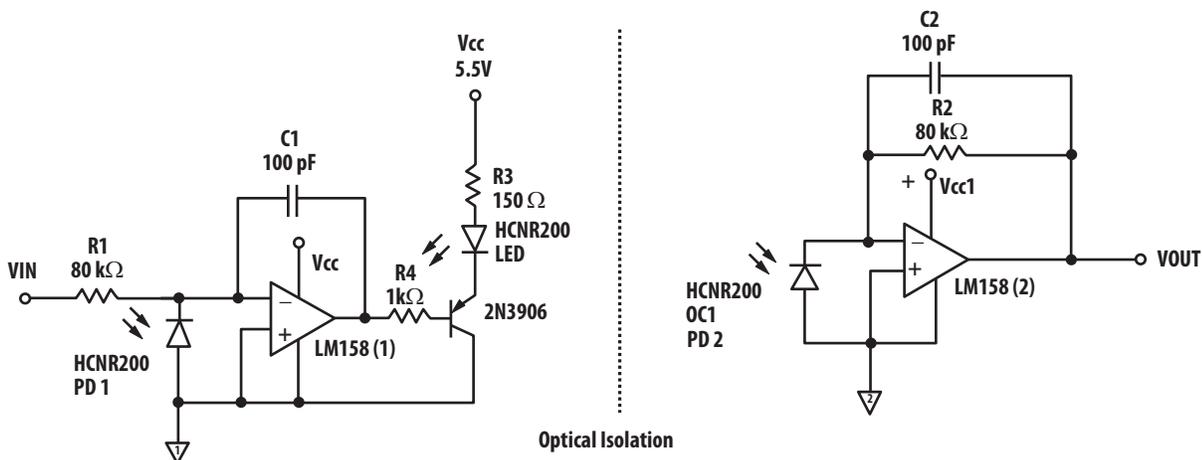


Figure 1. Positive Polarity Input Voltage Analog Isolation Amplifier using the HCNR201 in Photovoltaic Mode

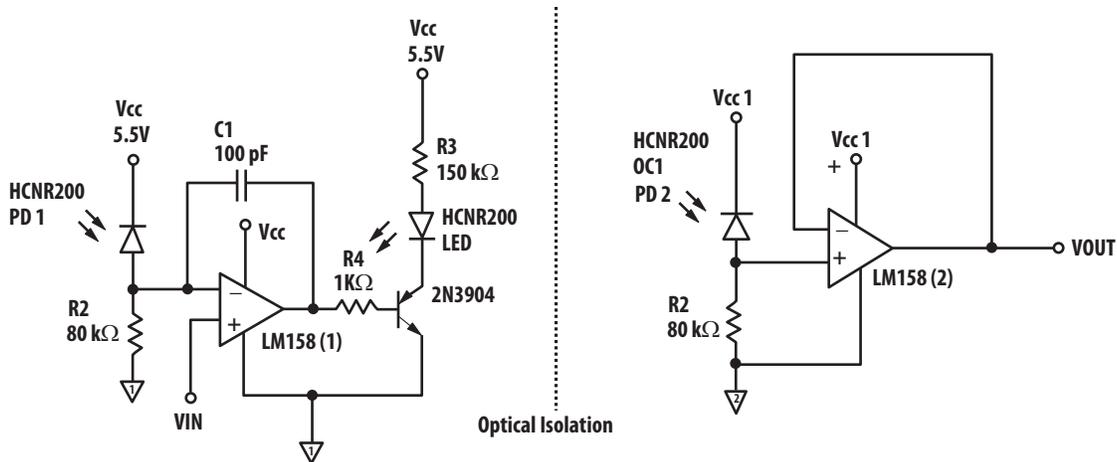


Figure 2. Positive Polarity Input Voltage Analog Isolation Amplifier Using the HCNR201 in Photo-Conductive Mode

Typically, the transfer gain  $K_3=1$ , and is  $\pm 5\%$  for the HCNR201 and  $\pm 15\%$  for the HCNR200. The input photo gain is represented by the  $K_1$  parameter in the data sheet and is defined as  $I_{PD1}/I_F$ . The data sheet for the HCNR201 lists this input current transfer ratio as (0.25 to 0.75)% for HCNR200 and (0.36 to 0.72)% for the HCNR201. As indicated in the data sheet for best linearity, the photodiode current is to be between 5 nA and 50  $\mu$ A. This implies that the  $V_{in}$  and R1 combination at the input should constrain the externally set maximum photodetector current at 50  $\mu$ A. However, higher photodetector current up to 100  $\mu$ A can be easily set at high LED currents close to 25 mA.

Figure 2 shows the HCNR201 biased in a photo-conductive mode of operation, where the photodiodes are forced into reverse bias. In reverse bias the photodiode capacitance is lower as the depletion regions are larger. Thus, for a higher band-width response it may be advantageous to use the photoconductive configuration. The equations to derive the transfer function are similar to the photo-voltaic mode discussed earlier. With R1 at 80  $\Omega$  an input voltage maximum of 4 V will keep the maximum photodiode current at 50  $\mu$ A to achieve the linearity indicated in the data sheet of the HCNR201. As noted before, photodiode currents up to 100  $\mu$ A or higher can be easily set if so desired.

### Bipolar Input Voltage Analog Circuit

Using similar concepts as developed for the positive-polarity input voltage analog amplifier discussed before, it is quite straightforward to develop a bipolar input voltage analog amplifier. Figure 3 shows the bipolar input voltage analog circuit using the HCNR201 in a servo feedback loop.

This bipolar input voltage circuit uses two HCNR200 or HCNR201 optocouplers. The top half of the circuit consisting of PD1, R1, DA, C1 and R4 Optocoupler 1 (OC1) LED is for the positive input voltages. The lower half of the circuit consisting of optocoupler 2 (OC2) PD1, R2, BB and R5. Optocoupler 2 (OC2) LED is for the negative input voltages.

The diodes D1 and D2 help reduce crossover distortion by keeping both amplifiers active during both positive and negative portions of the input signal. Balance control R1 at the input can be used to adjust the relative gain for the positive and negative input voltages. The gain control R7 can be used to adjust the overall transfer gain of the amplifier. The capacitors C1, C2, and C3 are the compensation capacitors for stability.

## Current to Voltage Converter

For measurement of very small currents such as transducer sensor currents, a simple analog current-to-voltage circuit can be designed as shown in Figure 4. This circuit uses two HCNR200 optocouplers. The input current can be of either polarity. The upper limit for the  $I_{IN}$  should be constrained to 50  $\mu\text{A}$  maximum to achieve the non-linearity specifications of 0.05% indicated in the data sheet.

The lower limit of the current measurement depends upon the maximum dark current associated with the photodiodes, which are approximately in the neighborhood of 100 pA maximum over temperature. The two HCNR200

devices in this configuration are essentially connected in an anti-parallel configuration. One HCNR200 then translates the positive input current to a positive voltage. The second HCNR200 translates the negative current into a negative output voltage.

The resistor R2 is chosen to give the full scale output voltage as:

$V_{out} = \pm I_{IN} R_2 = \text{full scale output voltage}$ . Thus R2 would be 100 k $\Omega$  at 50  $\mu\text{A}$  maximum input current for a full-scale output voltage of 5 V. Photodiode currents up to 100  $\mu\text{A}$  or higher can also be easily selected.

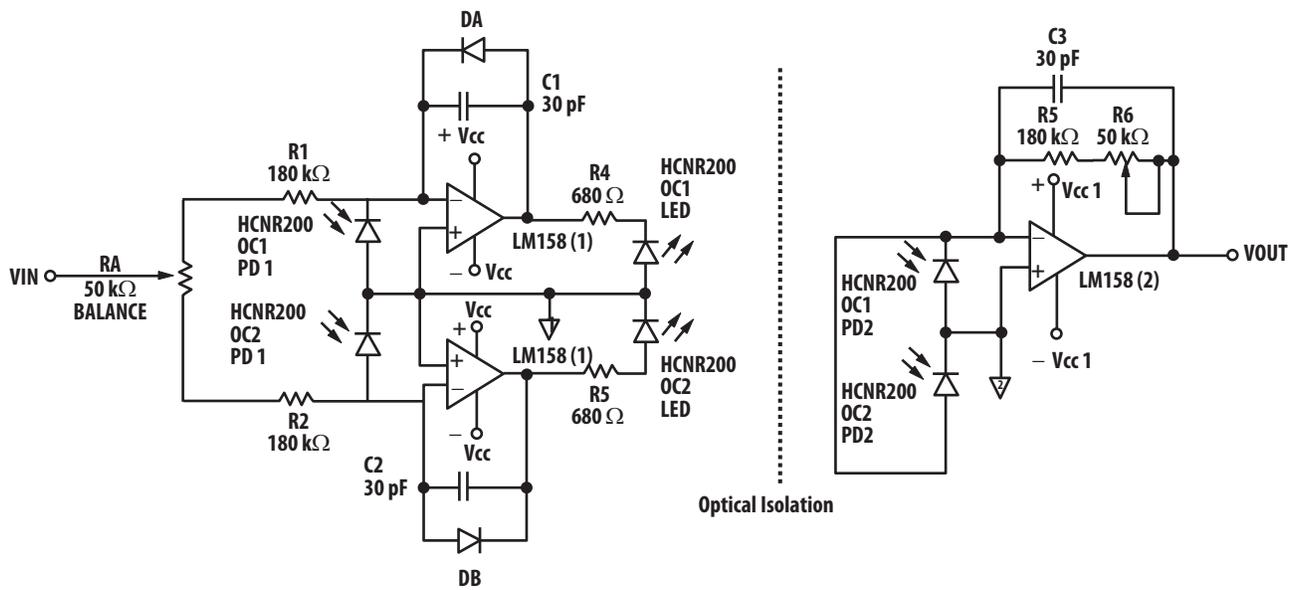


Figure 3. Bipolar Input Voltage Analog Isolation Amplifier using the HCNR201

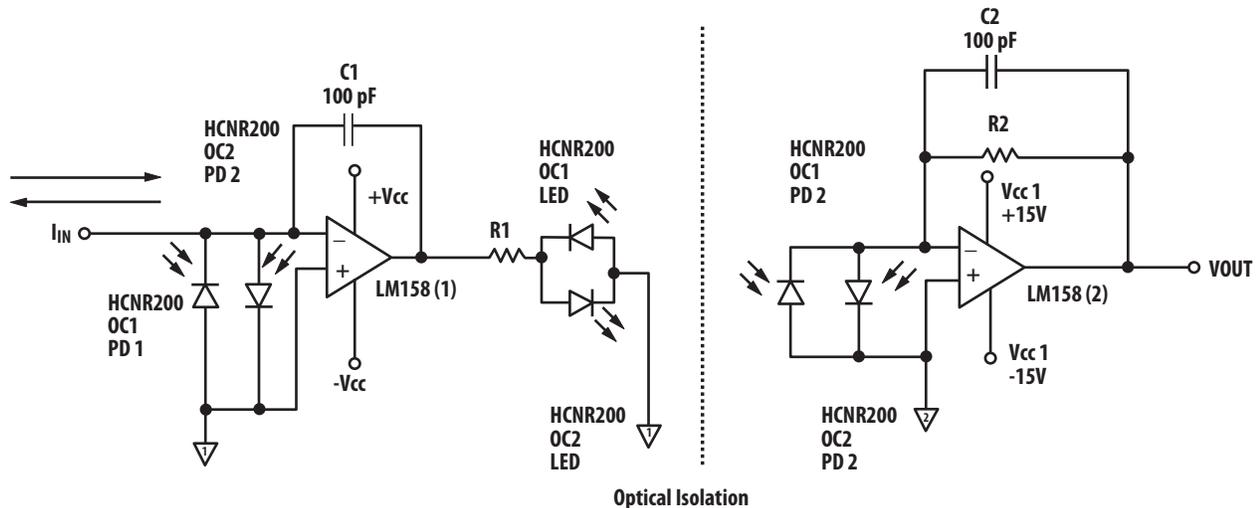


Figure 4. Current-to-Voltage Converter using the HCNR200

## Isolated 4-to-20 mA Analog Transmitter Circuit

Industrial manufacturing environments very often require measuring temperatures, pressures, or fluid levels in a harsh, electrically noisy environment. Transmitting signals through current instead of voltage could be advantageous in such an environment. Very often the distance between the sensor stage to a controller, typically a PLC or a microcontroller, can be a sizeable distance. Additional requirements in such an application could be for high voltage insulation or galvanic insulation for safety protection either of operators or expensive digital logic. Both of these critical requirements can be easily addressed through the use of optically isolated 4 to 20 mA transmitter and receiver circuits.

Figure 5 shows a 4-to-20 mA analog transmitter circuit designed around the HCNR201.

A unique feature of this circuit is that there is no need for an isolated power supply on the loop side of the optical circuit. The loop current generator supplies the power supply voltage. The zener Z1 establishes the voltage required by the loop-side op-amp. To establish the transfer function, the following equations are used:

$$I_{PD1} = V_{IN}/R_1$$

$K_3 = I_{PD2}/I_{PD1} = 1$  (by the transfer gain indicated in the data sheet)

The current division at the intersection of  $R_5$ ,  $R_4$ , and  $R_3$  establishes the photodiode current ( $I_{PD2}$ ) portion of the loop current. The resistors  $R_3$  and  $R_5$  are essentially in parallel and form the actual current divider. Thus,  $I_{PD2}$  can be written as

$$I_{PD2} = I_{LOOP} \cdot (R_5/(R_5 + R_3))$$

Solving these equations yields the transfer function as

$$K_3 \cdot V_{IN}/R_1 = I_{LOOP} \cdot (R_5/(R_5 + R_3))$$

$$I_{LOOP}/V_{IN} = K_3 \cdot (R_5 + R_3)/(R_5 R_1)$$

The resistor values have been so selected in this example that when input voltage is 0.8 V the loop current is 4 mA, and when the input voltage is 4 V, the loop current is

20 mA. This assumes that the transfer function  $K_3$  equals 1, which is the case typically as indicated in the data sheet for the HCNR201.

## Isolated 4-to-20 mA Analog Receiver Circuit

The 4-to-20 mA receiver circuit is similar in construction to the 4-to-20 mA transmitter circuit discussed earlier. In the receiver case, the loop current is received at the input of the receiver, and the output is a linear voltage representation of the input loop current. Figure 6 shows the receiver circuit.

Once again, no isolated power supply is needed on the loop side of the receiver circuit, as the power supply is established by the source supplying the loop current. The zener  $Z_1$  establishes the 5 V level for the op-amp power supply. The loop current is split at the junction of  $R_3$  and  $R_2$  and  $PD_1$ . The resistors  $R_1$  and  $R_3$  are essentially in parallel, as there is zero volts across the photodiode diode ( $PD_1$ ). The servo op-amps forces zero volts across  $PD_1$ , and thus  $R_1$  and  $R_3$  form the current divider for the loop current.

The transfer function for the receiver circuit can be established by observing the following equations

$$I_{PD1} = I_{LOOP} \cdot (R_3/(R_3 + R_1))$$

$$K_3 = I_{PD2}/I_{PD1}$$

$$V_{OUT} = I_{PD2} \cdot R_5$$

Solving these equations leads us to the transfer function as

$$V_{OUT}/R_5 = K_3 \cdot I_{LOOP} \cdot (R_3/(R_3 + R_1))$$

$$V_{OUT}/I_{LOOP} = K_3 \cdot R_5 \cdot R_3/(R_3 + R_1)$$

The resistor values shown in the receiver circuit are scaled such that when loop current is 4 mA the output voltage is 0.8 V. When the loop current is 20 mA the output voltage is 4 V. This again assumes that  $K_3$  (transfer function) equals 1 which is typically the case as indicated in the data sheet for the HCNR201.

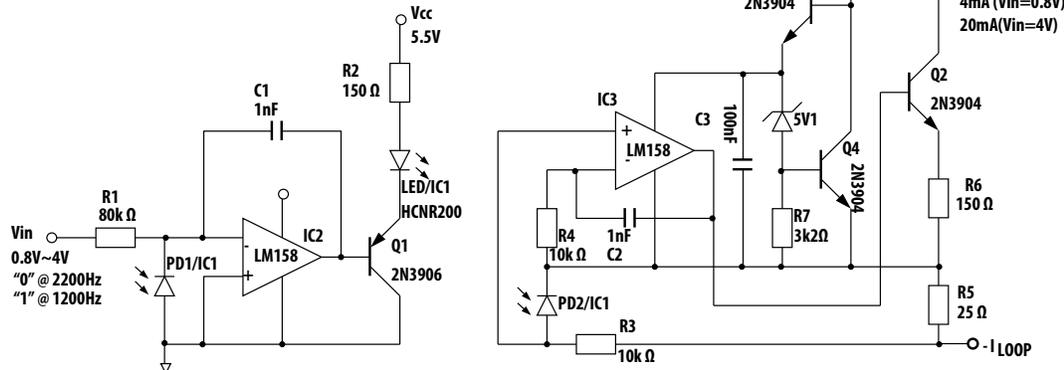


Figure 5. 4 to 20 mA HCNR201 transmitter circuit

## Wide Bandwidth Video Analog Amplifier

For wide-bandwidth video analog applications an amplifier design is shown in Figure 7. This is an AC input coupled and AC output coupled circuit. The LED input current  $I_F$  is set at the recommended 6 mA for the HCPL-4562 or 10 mA for the HCNW4562 by selecting an appropriate value for the  $R_4$ . If the  $V_{CC1}$  on the input side is 5 V the voltage  $V_B$  established by the resistor divider  $R_1$  and  $R_2$  at the base of Q1 (neglecting base current drop across  $R_3$ ) is approximately 1.16 V. This establishes the voltage  $V_E$  at the emitter of Q1 as 0.56 V. Adjust  $R_4$  to set the recommended LED current at 6 mA. With 0.56 V at  $V_E$  the resistor  $R_4$  is selected to be approximately 93  $\Omega$  for 6 mA of  $I_F$ .

With a  $V_{CC2}$  supply between (9 to 12) V, the value of  $R_{11}$  is selected to keep the output voltage at midpoint of the supply, approximately 4.25 V with the collector current  $I_{CQ4}$  of Q4 at approximately 9 mA.

Where  $R_{11}$  is the parallel combination of  $R_{11}$  and load impedance and  $f_{T4}$  is the unity gain frequency Q4. From this equation one can observe that to maximize the bandwidth one would want to increase the value of  $R_{11}$  or reduce the value of  $R_9$  at a constant ratio of  $R_9/R_{10}$ .

$$I_{CQ4} \leq 4.25 \text{ V} / 470 \Omega \leq 9 \text{ mA}$$

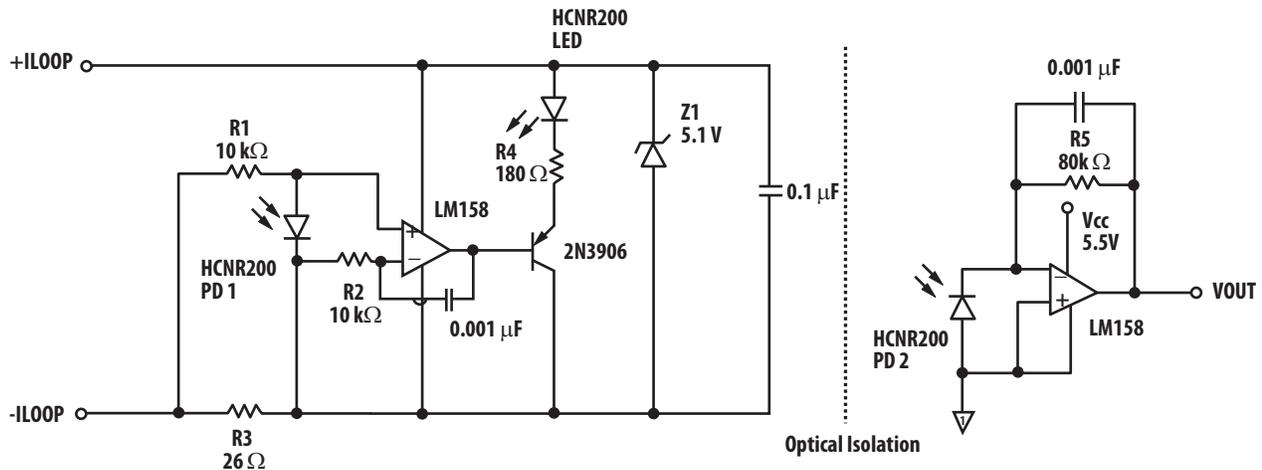


Figure 6. Isolated 4-to-20 mA Analog Receiver Circuit using the HCNR200

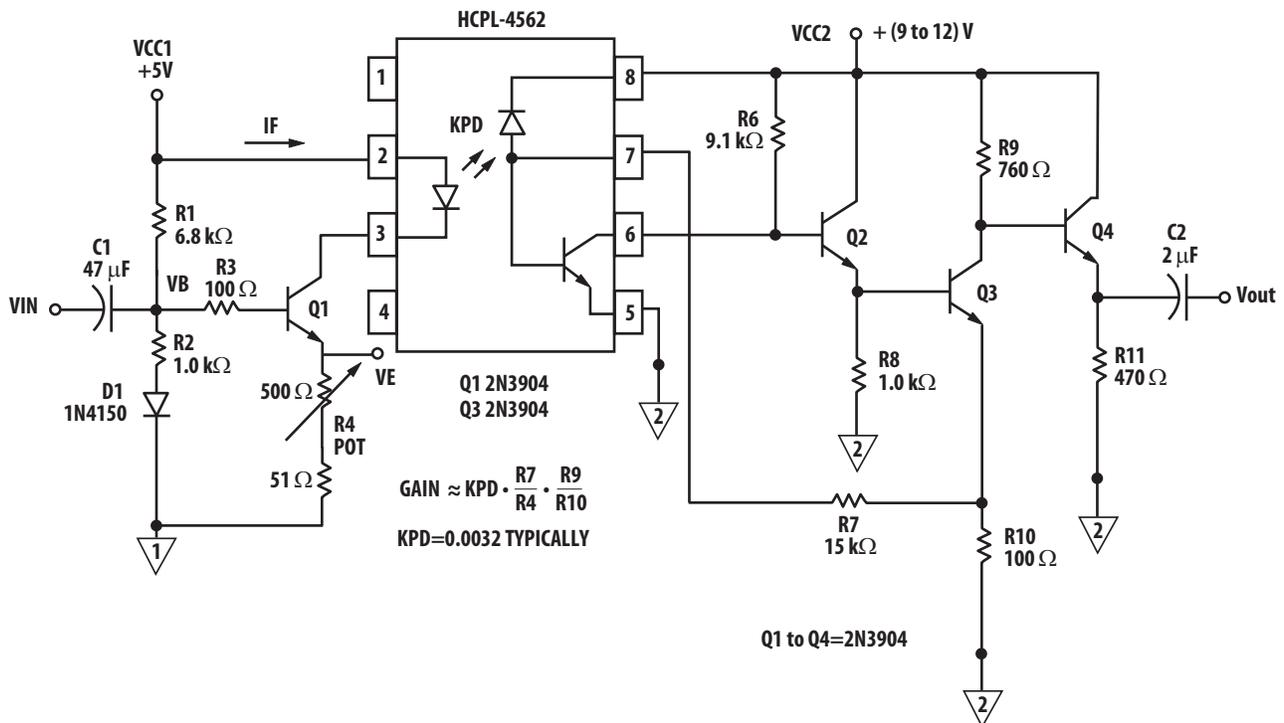


Figure 7. Wide Bandwidth Analog Isolation Amplifier Using the HCPL-4562

The small signal model of the bipolar transistors can determine the overall voltage gain of the circuit and gain stages involved and is found to be

$$G_V \approx V_{OUT}/V_{IN} \\ \approx \partial I_{PB}/\partial I_F [R_7 R_9 / R_4 R_{10}]$$

Where  $\partial I_{PB}/\partial I_F$  is the base photocurrent gain (photodiode current gain) and is indicated as a typical of 0.0032 in the data sheet. Adjust resistor  $R_4$  to achieve the desired voltage gain. The voltage gain of the second stage (Q3) is approximately equal to

$$R_9 / R_{10} \cdot [1 + sR_9 (C_{CQ3} + 1/(2\pi R_{11} f_{T4}))]$$

### Optically Coupled Regenerative Audio Receiver

A simple optically coupled regenerative (OCR) RF audio receiver can be constructed using the HCPL-4562 where the tuning control and regenerative control are optically isolated from the rest of the receiver circuit.<sup>2</sup> Figure 8 shows one such regenerative detector design, where the RF from the antenna is optically coupled to the base of the oscillator transistor.

In this design the optocoupler's transistor is configured as a Colpitt's oscillator. The base current that controls the oscillation of the optocoupler output transistor (Q1) is supplied by the optical photon coupling from the input LED  $I_F$  modulation. The RF energy from the antenna is coupled to the LED by the tuned circuit formed by  $T_1$  and  $C_1$ . The 10 k $\Omega$  potentiometer provides the regeneration control at the input of the LED.

It is possible to connect an audio transformer directly in the collector circuit of Q1 to drive high sensitivity, high impedance headphones. However, in the design shown in Figure 8 the audio is recovered by a high impedance MOSFET transistor Q2. The tuned circuit (L1, C2) is connected to the gate of this infinite impedance MOSFET transistor Q2 which has a minimal loading impact on the tuned circuit. The audio voltage is developed across  $R_S$  (27 k $\Omega$ ). The simple RC filter formed by  $R_S$  and the 0.1  $\mu$ F capacitor filters out the RF component and passes the audio component to the headphones. If necessary, one can connect an additional amplification stage, along with further filtering, and an audio amplifier at the output to drive low impedance headphones.

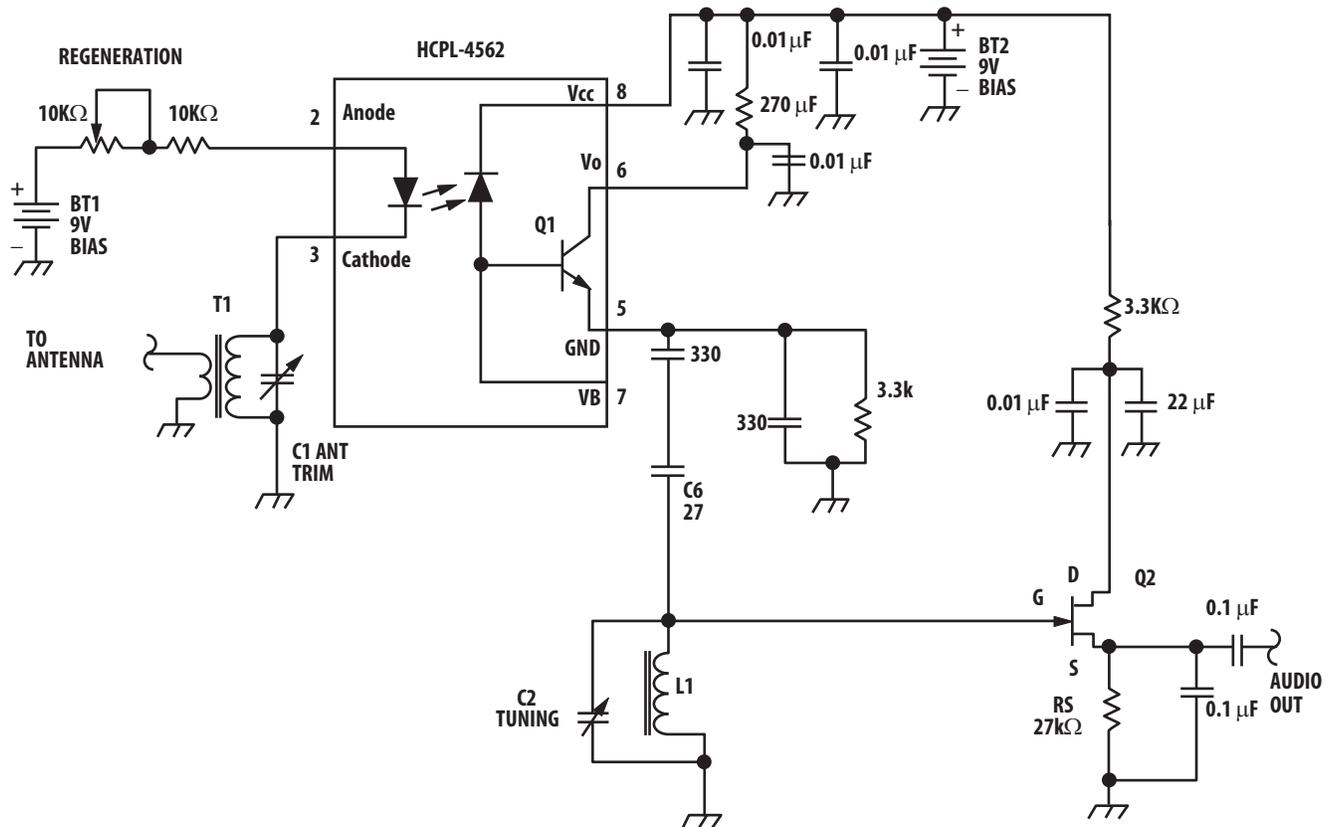


Figure 8. Optically Coupled Regenerative Audio Receiver

## Avago's Isolation Amplifiers

An optical isolation boundary in isolation amplifiers provides high common mode rejection capability. Sigma-Delta modulation and unique encoding/ decoding technologies provide high precision and stable performance. High performance relies on an integrated high-speed digital optocoupler to transmit a signal across the isolation boundary. Figure 9 is the functional block diagram. The HCPL-788J integrates the short circuit and overload detection commonly found in intelligent motor drives.

A second order  $\Sigma\text{-}\Delta$  modulator converts an analog input signal into a single-bit data stream, which is edge-triggered by an encoder. High speed encoded data is transmitted through the optical channel and is recovered to single-bit stream by a decoder. The digital-to-analog converter simply converts single-bit stream into very precise analog voltage levels. The final analog output voltage is recovered by filtering the DAC output. The filter was designed to maximize bandwidth while minimizing quantization noise generated by the sigma-delta conversion process. The overall gain of the isolation amplifier is determined primarily by matched internal temperature-compensated bandgap voltage references, resulting in very stable gain characteristics over time and temperature.

The typical performance, such as offset, gain tolerance, nonlinearity and temperature drift, can be guaranteed by a differential output. One external op-amp has three functions: to reference the output signal to the desired level (usually ground), to amplify the signal to appropriate levels, and to help filter output noise.

A single-pole output from the isolation amplifier, like  $V_{OUT+}$  to GND2, can be used to save costs by using fewer op-amps and other components.

The absolute output from the HCPL-788J smart amplifier is usually used to monitor AC current, regardless of current polarity. The absolute value output can directly connect to a microcontroller and simplify the design of the output signal circuit.

Shown in Figure 10, the HCPL-7860/786J isolated modulator has a direct Sigma-Delta signal output with modulation clock, which can be directly connected to a microprocessor and converted to 12-bit effective resolution digital data.

Table 1 shows an overview of isolation amplifiers.

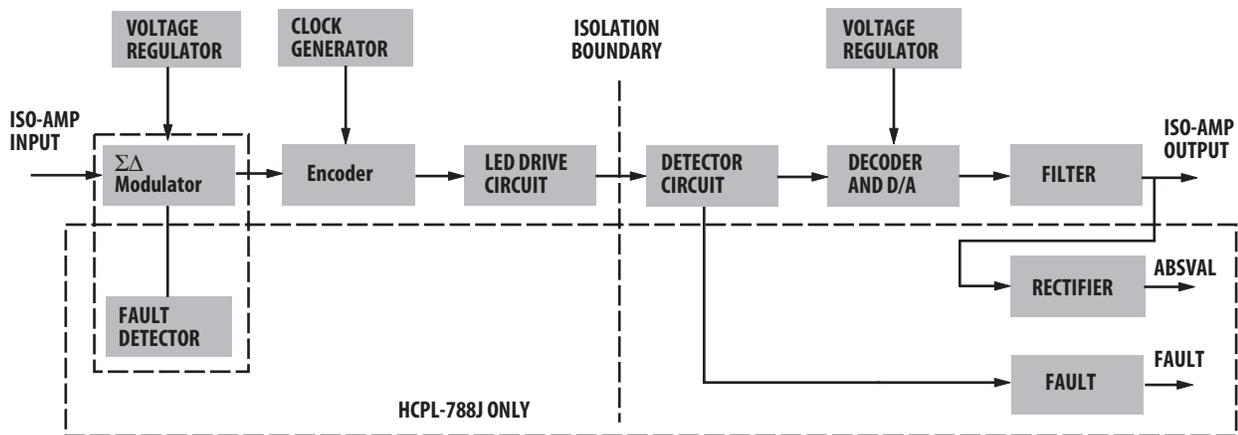


Figure 9. HCPL-7800/7840/788J Block Diagram

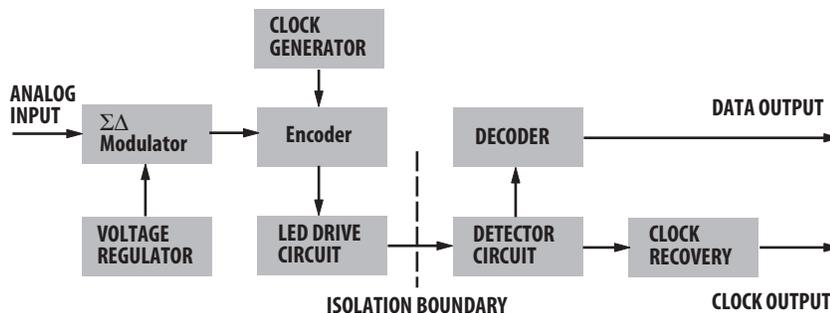


Figure 10. HCPL-7860/786J Block Diagram

**Table 1. Specifications Overview of Isolation Amplifiers.**

Isolated Amplifier, HCPL-	7800	7800A	7840	788J
Gain Tolerance, %	±3	±1	±5	±5
Max. Input Offset Voltage, mV	3	3	3	3
Max. Input Offset Drift Vs Temperature, mV/°C	10	10	10	10
VOUT 100 mV Max. Nonlinearity, %	0.2	0.2	0.2	0.4
Typ. Gain Drift Vs Temperature, ppm/°C	250	250	250	50
Max. Prop Delay, ms	9.9	9.9	9.9	20
Min. CMR at V <sub>CM</sub> = 1 kV, kV/ms	10	10	10	10
Package Type	DIP8	DIP8	DIP8	SO16
IEC/EN/DIN EN 60747-5-2 [V <sub>IORM</sub> ], V <sub>PEAK</sub>	891 <sup>[1]</sup>	891 <sup>[1]</sup>	891 <sup>[1]</sup>	891 <sup>[1]</sup>
UL [V <sub>ISO</sub> ], V <sub>RMS</sub>	3750	3750	3750	3750

Isolated Modulator, HCPL-	7860	786J
Max. Offset Drift Vs. Temperature, mV/°C	10	10
Max. Internal Reference Voltage Matching Tolerance, %	1	2
Min. CMR at V <sub>CM</sub> = 1 kV, kV/ms	15	15
Package Type	DIP8	SO16
IEC/EN/DIN EN 60747-5-2 [V <sub>IORM</sub> ], V <sub>PEAK</sub>	891 <sup>[1]</sup>	891 <sup>[1]</sup>
UL [V <sub>ISO</sub> ], V <sub>RMS</sub>	3750	3750


Note:

1. Option 060 is needed

## General Voltage Sensing

With Avago isolation amplifiers, a designer can simply eliminate extra noise when sensing AC or DC voltage. A high voltage source  $V_s$  (Figure 11) is divided by resistors  $R_s$  and  $R_1$  to get a typical voltage signal  $\pm 200$  mV from the formula:

$$V_{in} = V_s R_s / (R_s + R_1)$$

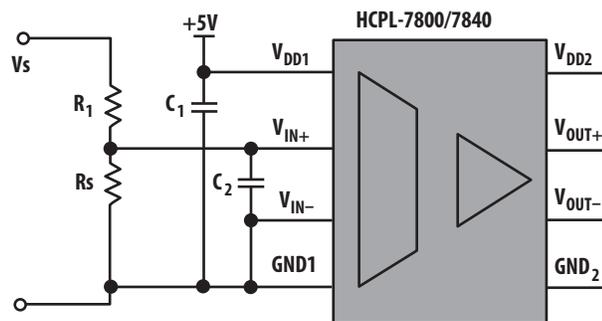

**Figure 11. General Voltage Sensing Circuit**

The  $R_s$  value should be relatively small to match with the isolation amplifier's input impedance, and to keep bias current relatively low which does not affect the accuracy of measurement. For example, the HCPL-7840 input impedance is 500 k $\Omega$  and a less than 1 k $\Omega$   $R_s$  will have 0.4  $\mu$ A peak bias current.

A capacitor  $C_1$  is connected as a low-pass filter to protect the isolation amplifier from voltage transients on the input signal. To obtain higher bandwidth, the capacitor  $C_1$  can be reduced, but it should not be reduced much below 1000 pF to maintain gain accuracy of the isolation amplifier.

A single-pole output between  $V_{OUT+}$  to GND<sub>2</sub> is usually used for general voltage sensing at low saving cost.

## General Current Sensing

A large current source can be sensed by a shunt resistor  $R_S$ , which converts the current to a voltage signal,  $V_{in} = I_S R_S$  (Figure 12).

For example, to monitor a single phase 240 VAC/1.2 kW lamp current, its peak current is:

$I_S = \pm(5 \cdot 1.414) \text{ A} = \pm 7.07 \text{ A}$ .  $R_S$  is calculated at  $28 \text{ m}\Omega$  while the peak current input voltage is  $\pm 198 \text{ mV}$ . This resistor results in a power dissipation less than  $1/4 \text{ W}$ .

The power supply  $V_{DD1}$  in input side of optocoupler can be available from the rectified and regulated AC line, but the output side power supply  $V_{DD2}$  must be isolated from the AC line.

A  $39 \Omega$  resistor  $R_1$  and bypass capacitor  $C_2$  are connected to filter voltage transients from the input signal.

A single-pole output between  $V_{OUT+}$  to  $GND_2$  is usually used for general current sensing at low cost.

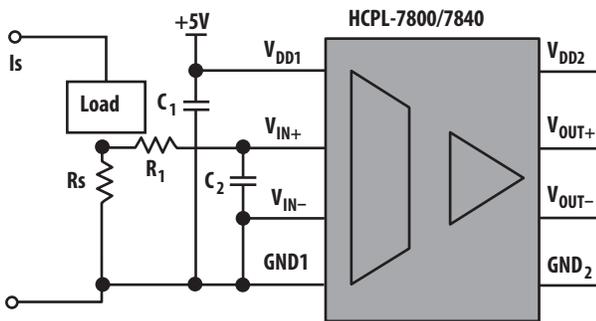


Figure 12. General Current Sensing Circuit

## Motor Current Sensing

Inverter or servo motor drivers implement vector control fast and accurately with two modern control loops: position feedback by an optical encoder and current feedback by an optical isolated amplifier.

Optical isolated amplifiers directly measure phases or rail current, replacing conventional indirect measurement through transformer or Hall Effect sensor. Users have recognized the significant advantages optocouplers offer: standard IC packages, high linearity, and low temperature drift. These features provide opportunities to make a compact, precise and reliable motor driver.

A typical application circuit in Figure 13 mainly consists of a shunt resistor, isolated amplifier and low cost op-amp.

The maximum shunt resistance  $R_S$  can be calculated by taking the maximum recommended input voltage and dividing by the peak current that should be seen during normal operation. For example, if a motor will have a maximum RMS current of  $30 \text{ A}$  and can experience up to  $50\%$  overloads during normal operation, then the peak current is  $63.3 \text{ A} (= 30 \cdot 1.414 \cdot 1.5)$ . Assuming a maximum input voltage of  $200 \text{ mV}$ , the maximum value of shunt resistance in this case would be about  $30 \text{ m}\Omega$ .

The particular op-amp used in the post-amp circuit is not critical. However, it should have low enough offset and high enough bandwidth and slew rate so that it does not adversely affect circuit performance. The gain is determined by resistors  $R_4$  through  $R_7$ , assuming that  $R_4 = R_5$  and  $R_6 = R_7$ , the gain of the post-amplifier is  $R_6/R_4$ .

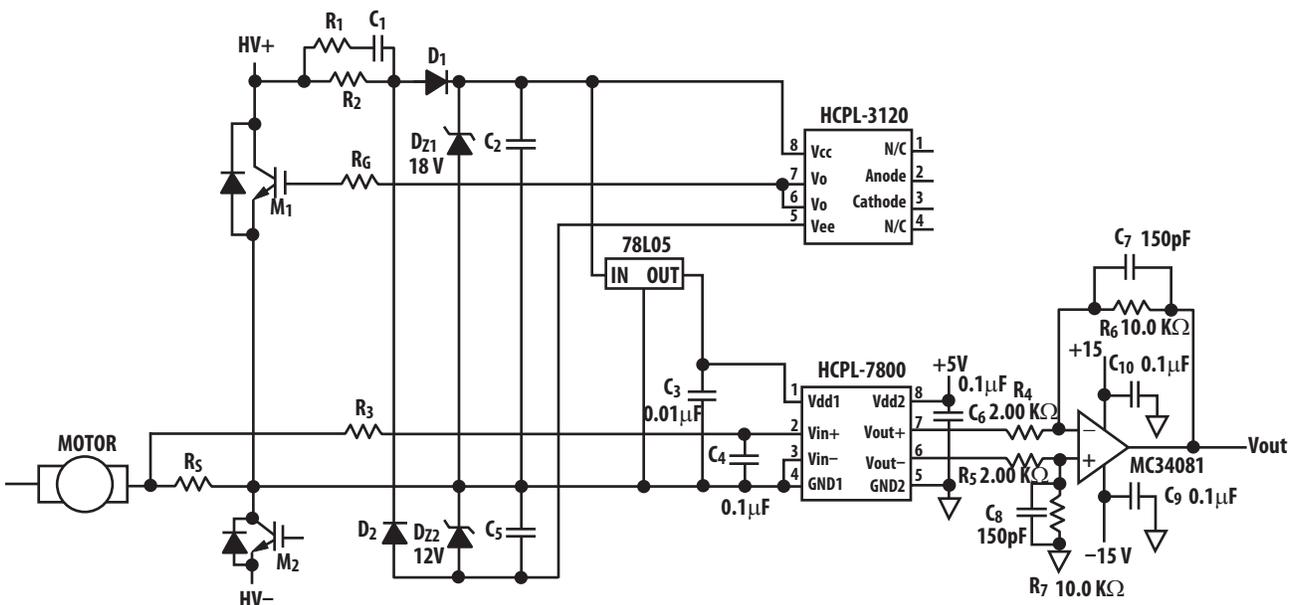


Figure 13. Motor Current Sensing Circuit

A bootstrap power supply is usually used to reduce cost and size in a motor driver. It eliminates the need for an isolated power supply or a DC converter. A bootstrap power supply for the high side of a half bridge is shown in Figure 5. When designing a bootstrap power supply, the bootstrap components,  $R_1$ ,  $R_2$ ,  $C_1$  and  $C_2$ , must be chosen to sufficiently power its load – the isolated half-side of gate driver and current sensing optocouplers.

When the lower IGBT is on, rail voltage goes through  $R_1$ ,  $R_2$  and  $C_1$  to charge capacitor  $C_2$  up to 18 V and meanwhile supply the HCPL-3120 and the regulator, which powers the current sensor. When the lower IGBT is off,  $C_2$  discharges and distributes its current to the gate driver and 78L05 regulator. The threshold voltage of the bootstrap power supply is 15 V, which is required by the gate driver (HCPL-3120).

When the lower IGBT is off, the stored energy on  $C_1$  will discharge to  $C_5$ , which together with  $D_{z2}$  generates a negative voltage source.

A bootstrap power supply for the low side of the half bridge is identical to the high side circuit.

## Conclusion

This paper has outlined and highlighted the wide scope and applications that are now possible using sophisticated and highly linear optocouplers. Designers can now choose and select an appropriate analog optocoupler available from Avago Technologies that meets their analog design criteria. This includes high common mode rejection capable current or voltage sensing optocouplers such as the HCPL-7800A or the HCPL-788J. Or the high linearity optocouplers such as the HCNR201. Or the high bandwidth optocouplers such as the HCPL-4562.

## References

- 1 *Photodiode Amplifiers: Op Amp Solutions*, Jerald G. Graeme, McGraw-Hill, New York, 1996.
- 2 "The OCR Receiver," QST, Daniel Wissell, N1BYT, June 1998, pp 35-38.
- 3 "Designing with Avago Technologies Isolation Amplifiers" Avago Technologies, Application Note 1078, Publication No. 5965-5976E, 1999.
- 4 "Optocouplers for Variable Speed Motor Control Electronics in Consumer Home Appliances" Jamshed N. Khan, Avago Technologies, White Paper, Publication No. 5980-1297E, 2000.
5. "Motor Drive and Inverter Design Using Optocouplers" Joe Pernyeszi, Mike Walters and Jason Hartlove, Proceeding of PCIM, pp. 397-406, 1995.
6. *Optocoupler Designer's Guide*, Avago Technologies, Publication No. 5988-4082EN, 2002.
7. "Isolation Amplifiers Compared to Hall Effective Devices for Providing Feedback in Power-Conversion Applications" D. Plant, Proceeding of the Second Small Motor International Conference (SMIC), pp. 353-358, 1996.

For product information and a complete list of distributors, please go to our web site: [www.avagotech.com](http://www.avagotech.com)