



# **PEX 8508**

## **Quick Start Hardware Design Guide**

---

**Version 1.1**

**May 2006**

**Website:** <http://www.plxtech.com>

**Email:** [apps@plxtech.com](mailto:apps@plxtech.com)

**Phone:** 408 774-9060

800 759-3735

**Fax:** 408 774-2169

© 2006 PLX Technology, Inc. All rights reserved.

PLX Technology, Inc. retains the right to make changes to this product at any time, without notice. Products may have minor variations to this publication, known as errata. PLX assumes no liability whatsoever, including infringement of any patent or copyright, for sale and use of PLX products.

PLX Technology and the PLX logo are registered trademarks of PLX Technology, Inc.

Other brands and names are the property of their respective owners.

Order Number: PEX 8508-SIL-DG-P1-1.1

Printed in the USA, May 2006

# Table of Contents

1.	PEX 8508 Interfaces.....	5
2.	PEX 8508 High-Speed Link Interface .....	7
2.1.	Programmable SerDes De-Emphasis .....	7
2.2.	Programmable SerDes Driver Current .....	7
2.3.	Adjustable VTT Settings.....	7
2.4.	Layout Considerations .....	8
2.5.	Testability Considerations .....	8
3.	Reference Clock Circuitry .....	8
3.1.	Spread Spectrum Clocking (SSC).....	9
3.1.1	Spread Spectrum Clock Isolation .....	9
4.	Reset Circuitry .....	11
5.	EEPROM Interface .....	11
6.	I2C Interface .....	12
7.	Hot Plug Circuitry .....	13
8.	D3-cold Power Management Support (L2 link state) .....	14
9.	Power Supplies, Power Decoupling, and Power Sequencing .....	16
9.1.	Power Supplies .....	16
9.2.	Board Level Decoupling .....	17
9.3.	Power Sequencing .....	19
10.	PEX 8508 Miscellaneous Signal Groups .....	19
10.1.	Configuration Strapping Pins .....	19
10.2.	PCI Express Lane Good Indicators .....	19
10.3.	JTAG Interface Signals .....	20

## Figures

Figure 1.	PEX 8508 Interfaces.....	6
Figure 2.	Return current path utilizing stitching vias .....	8
Figure 3.	PEX_REFCLKP/N Implementation Example.....	9
Figure 4.	Single reference clock scheme (STRAP_SSC_XING_ENA pulled low) .....	10
Figure 5.	Dual reference clock, SSC crossing scheme (STRAP_SSC_XING_ENA pulled high) .....	11

Figure 6. PEX 8508 32-Kbyte SPI EEPROM Interface.....	12
Figure 7. PEX 8508 64-Kbyte SPI EEPROM Interface.....	12
Figure 8. I2C bus connectivity.....	13
Figure 9. PEX 8508 Hot Plug Controller Interface .....	14
Figure 10. Supplying VTT_PEX during D3-cold.....	15
Figure 11. Power Plane impedance vs. frequency .....	18
Figure 12. Generic JTAG interface .....	20

# Introduction


This design note is intended to provide PLX Technology's PCI Express switch users with an overview of the PEX 8508 from a device interface perspective, and to provide examples of how to connect to the various interfaces.

## 1. PEX 8508 Interfaces

The PEX 8508 device is a 8-lane, 5-port PCI Express switch designed for high availability, high performance systems. The PEX 8508 signal interfaces can be grouped into several functional blocks. These blocks are as follows:

- PCI Express 2.5Gbps link interface signals (per port)
- Hot plug controller interface signal(s) (per port)
- Reference clock input(s)
- Fundamental Reset input
- EEPROM interface signals
- JTAG controller interface signals
- Strapping pins
- Lane status indicator signals
- Power and ground pins
- I2C Interface

Figure 1 shows the external pin interface for the PEX 8508 device. The PEX 8508 has eight PCI Express lanes, which consist of both transmit and receive differential pairs (four physical signals).

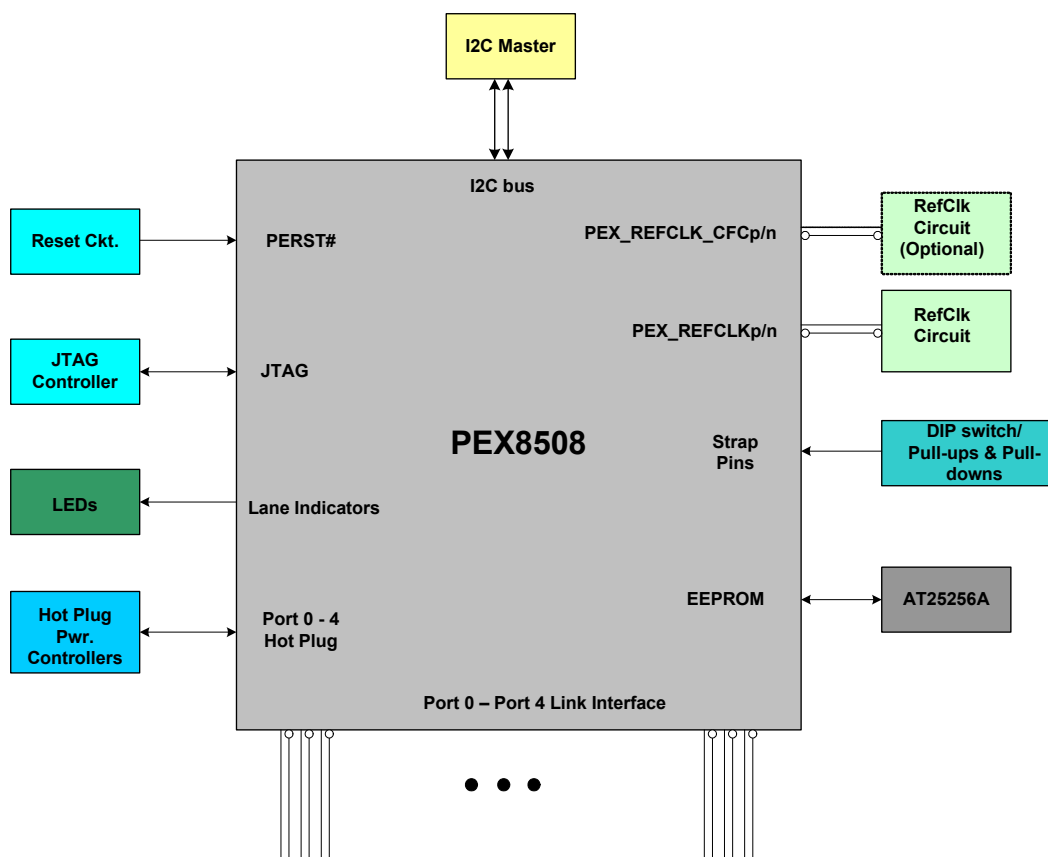

**Figure 1. PEX 8508 Interfaces**

The PEX 8508 allow multiple lanes to be logically grouped through strapping pins or EEPROM configuration. These lanes constitute a common signal interface between two PCI Express ports (i.e. a PCI Express link).

## 2. PEX 8508 High-Speed Link Interface

Each lane on the PEX 8508 is implemented using a SerDes I/O (serializer/deserializer). The line rate of each transmitter is 2.5Gbps; therefore, the bit time or unit interval is 400ps. The rise and fall time of the transmitter is near 100ps for transition bits; therefore, the knee frequency of the signal will be around 3.5 GHz ( $f_{3db} = 0.35/t_{rise}$ ). At these frequencies, PCB transmission lines behave like low-pass filters due to frequency dependant dielectric and conductor losses. It is important to ensure that the physical interconnect between devices produces as little signal loss and jitter as possible.

PCI Express serial links are AC coupled transmission lines. AC coupling capacitors are required on all transmitters to isolate the DC component of a signal between a transmitter and receiver. PCI Express signal transmission utilizes 8b/10b encoding; therefore, the minimum frequency content of a signal is 125MHz. In order to allow the lower frequency components of the signal to pass with minimal loss, AC coupling capacitors must be within the range of 75 nF– 200 nF. For minimizing impedance discontinuities and signal loss, 0402 or 0603-size ceramic capacitors should be used.

The PEX 8508 provides a number of ways to optimize the SerDes driver characteristics to aid the system designer in trying to meet the needs of his/her application.

### 2.1. Programmable SerDes De-Emphasis

Each SerDes driver contains a first order equalization function that allows for the de-emphasis of non-transition bits within a data pattern. The PEX 8508 provides two 32-bit registers (Memory addresses: BAR0+254h and BAR0+258h), that partition into eight 4-bit fields. These fields allow the equalization ratio to be programmed through EEPROM loading or register writes. The default value coming out of reset is 8h (all 4-bit fields), which sets non-transition bit de-emphasis to -3.35 dB. Equalization is intended to help reduce Inter Symbol Interference (ISI) and loss by providing a stronger drive current for transition bits compared to non-transition bits. This helps to boost the higher frequency components of the transmitted data pattern, in order to counter the low-pass filter effects of FR4 transmission lines.

### 2.2. Programmable SerDes Driver Current

The PEX 8508 also provide programmable driver current. The PEX 8508 contains one 32-bit register (Memory addresses: BAR0+248h) partitioned into eight 2-bit fields. These registers allow the driver's nominal current ( $I_{nom}$ ) to be set at 10mA, 20mA or 28mA. The default value coming out of power-on reset is 0h (20mA). This default value can be overwritten via EEPROM load or through register writes.


The actual driver current ( $I_{tx}$ ) is a scaled multiple of the nominal current. The PEX 8508 provides two 32-bit registers, partitioned into eight 4-bit fields (Memory addresses: BAR0+24Ch and BAR0+250h) that allow for a programmable ratio of actual current to nominal current. These registers allow the actual current to be linearly scaled up to 135% or scaled down to 60% of the nominal current. The default value coming out of reset is 0h ( $I_{tx}/I_{nom} = 1.00$ ). This feature can be used to reduce power consumption in applications where the physical link is short, or to boost driver current for longer transmission lines. The transmitter's output voltage swing is determined by multiplying the fixed lane termination resistance of both the transmitter and receiver (25  $\Omega$ ) by the actual driver current; hence, the voltage swing can be reduced by lowering the programmable driver current ( $V_{TX-DIFFp} = I_{TX} * Z_T/2$ ). Note that  $V_{TX-DIFFp}$  is the single-ended voltage swing.

### 2.3. Adjustable VTT Settings

In addition to reducing the driver current, the SerDes termination supply voltage (VTT\_PEX[5:0]) can range from 1.2V up to 1.8V. This supply voltage determines the driver's common mode voltage and limits the output voltage swing ( $V_{TX-CM} = V_{TT} - V_{TX-DIFFp}$ ). The system designer should simulate their design to find out the best fit for their application.

## 2.4. Layout Considerations

Differential signaling reduces the amount of return current that will flow on the pair's adjacent reference plane. This helps to reduce impedance discontinuities due to non-ideal return current paths, and to reduce EMI. When laying out differential pairs, pay attention to the pair's common mode return current path. If a signal pair transitions from one signal layer to another signal layer, make sure that there is a low inductance path between the corresponding reference planes for the return current. If the signal is referencing a ground plane, and transitions through a signal via to another layer that references a different ground plane, provide a ground or 'stitching' via (connecting the ground planes) near the signal's via to allow the return current to stay close to the signals. BGA pin field ground connections and connector pin field ground connections provide ground vias for signals that change layers near those devices. Figure 3 shows an example of how return currents can utilize stitching vias to change reference planes.

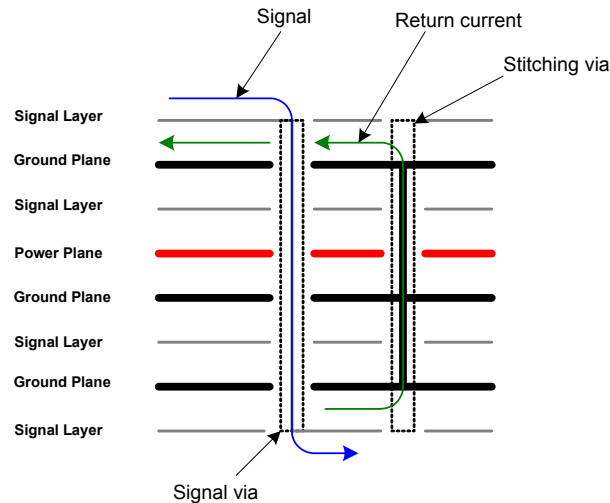

**Figure 2. Return current path utilizing stitching vias**

If a signal is referencing a DC power plane and changes layers to reference a DC ground plane, stitching capacitors can be placed near the signal transition points to provide an AC return path from a given reference DC power plane to the reference ground plane.

## 2.5. Testability Considerations


System designers should consider testability issues when laying out a PCI Express interconnect. For example, add-in card and system board designers might require the ability to use a logic analyzer between two devices. Since, the two devices can be physically separated (one on the system board, the other on the add-in card), a logic analyzer can be placed in-between the two PCI Express ports. Embedded system designers, whose systems integrate both devices on the same board, might consider the addition of a Mid-bus footprint in the routing path. Keep in mind that mid-bus footprints can add additional jitter and loss; therefore, a system designer should account for these effects when assessing their jitter and loss budgets. Additional information regarding Mid-bus footprints and equipment can be found at various PCI Express test equipment manufacturers such as Tektronix, CATC, Catalyst and Agilent.

## 3. Reference Clock Circuitry

PEX\_REFCLKp/n and PEX\_REFCLK\_CfCp/n are differential CML (Current Mode logic) clock inputs that receives a 100MHz (+/-300ppm) clock source. Each receiver input has an internal biasing circuit and an integrated 110  $\Omega$  differential termination. The biasing circuit sets the receiver's common mode voltage to 0.65V. The PEX 8508 reference clock input must be AC coupled to isolate the driver and



receiver DC common mode voltages. The recommended value for AC coupling capacitors on the reference clock input is 0.01  $\mu$ F – 0.1  $\mu$ F.

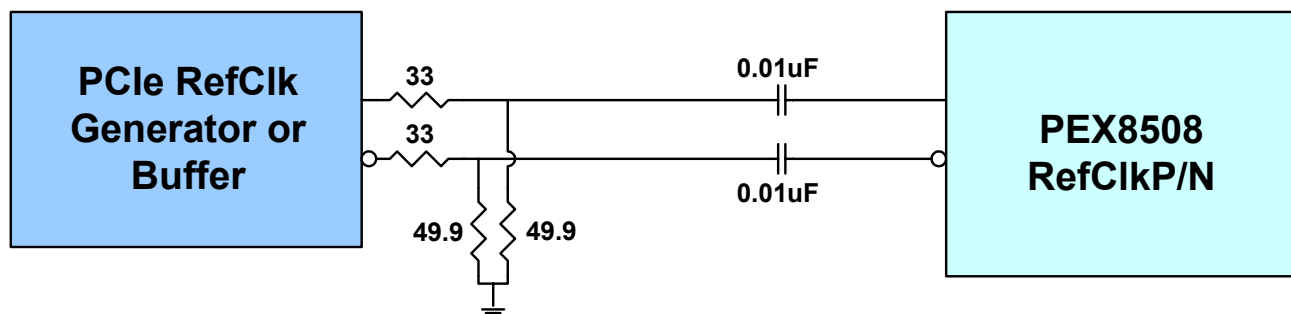

**Figure 3. PEX\_REFCLKP/N Implementation Example**

A number of vendors, such as Integrated Circuit Systems (ICS), provide PCI Express RefClk generators and buffers. The system designer should carefully select a synthesizer/buffer that meets the PCI Express reference clock jitter requirements.

### 3.1. Spread Spectrum Clocking (SSC)

Many PCI Express systems implement spread spectrum clocking in order to minimize EMI by spreading the spectral energy of the clock signal over a wide frequency band. In SSC systems, PCI Express components generally need to use a reference clock provided by the same source. This allows a transmitter PLL and receiver clock recovery function (CDR) to track the modulation frequency and stay in sync with each other. If only one side of the link uses a SSC reference clock and the other side does not, the transmitter and receiver circuits will not be able to properly track one another. For example, if a system designer implements a PCI Express add-in card that interfaces to an SSC system and also has a cable connection to a downstream card that is utilizing a constant frequency clock source (CFC), the downstream interface will not link-up. To solve this problem, a system designer using the PEX8508 can either use the SSC isolation feature (explained in section 3.1.1) or provide a means to pass the SSC clock to the downstream component.

#### 3.1.1 Spread Spectrum Clock Isolation

The PEX 8508 provides a new feature that helps eliminate the issues that exist when trying to communicate between two different systems, where one or both of those systems use SSC clocking.

The PEX 8508 has the necessary buffering and logic required to allow the upstream port to operate using both an SSC clock and a constant frequency clock (CFC) source. This feature is enabled when the signal STRAP\_SSC\_XING\_ENA is pulled up to VDD33. In order to use the SSC isolation feature, the upstream port must be port 0, and its programmed port width must be x4.


Enabling this feature provides the benefit of allowing downstream components to operate using an independent CFC clock source. If a PEX 8508 is placed into a system that uses spread spectrum clocking, and the SSC isolation feature is enabled, the downstream ports of the PEX 8508 will be clocked by a CFC clock source. System designers can then connect to a remote system without the requirements of sharing a reference clock source. The remote system must utilize a CFC clock source that meets the PCI Express +/-300ppm requirements.

It is important to understand that there is a frequency relationship between the PEX\_REFCLKp/n and the PEX\_REFCLK\_CFCp/n clock sources to the PEX8508 when SSC isolation is used. The

PEX\_REFCLKp/n is expected to be slower at its peak frequency than the PEX\_REFCLK\_CFCp/n source. For example, if the PEX\_REFCLKp/n is a SSC clock, then it will down modulate -0.5% at a rate between 30-33kHz. This means the frequency will change from 100MHz (+/-300ppm) down to 99.5MHz (+/-300ppm) and back to 100MHz over a period of 30-33.33 $\mu$ s. At the point where PEX\_REFCLKp/n is at it's maximum frequency (100MHz +/-300ppm), it is expected that the PEX\_REFCLK\_CFCp/n source be faster. If the PEX\_REFCLKp/n has a peak frequency of 100MHz +200ppm, then the PEX\_REFCLK\_CFCp/n should have a constant frequency of 100MHz +201ppm. It is best to design the PEX\_REFCLK\_CFCp/n source to operate as close to 100.03MHz as possible to guarantee reliable operation in a variety of systems. This can typically be accomplished by adjusting a source crystal's tuning capacitors. An example of this is the Integrated Circuit Systems ICS557-03 PCI Express Clock Generator. When using a 16pF-load crystal (as suggested in the manufacturers datasheet), providing tuning capacitors of 16pF will set the output frequency very close to 100.00MHz. By simply removing the two tuning capacitors, the output frequency will increase to slightly less than 100.03MHz.

Figure 4 depicts running the PEX 8508 using the standard distributed clocking scheme for PCI Express. If SSC isolation is not used, the PEX\_REFCLK\_CFCp/n inputs can be left unconnected.

Figure 5 demonstrates a mixed SSC and CFC system that might exist when utilizing PEX 8508's SSC isolation feature. NOTE: When SSC isolation is used, the SSC clock must be connected to PEX\_REFCLKp/n.

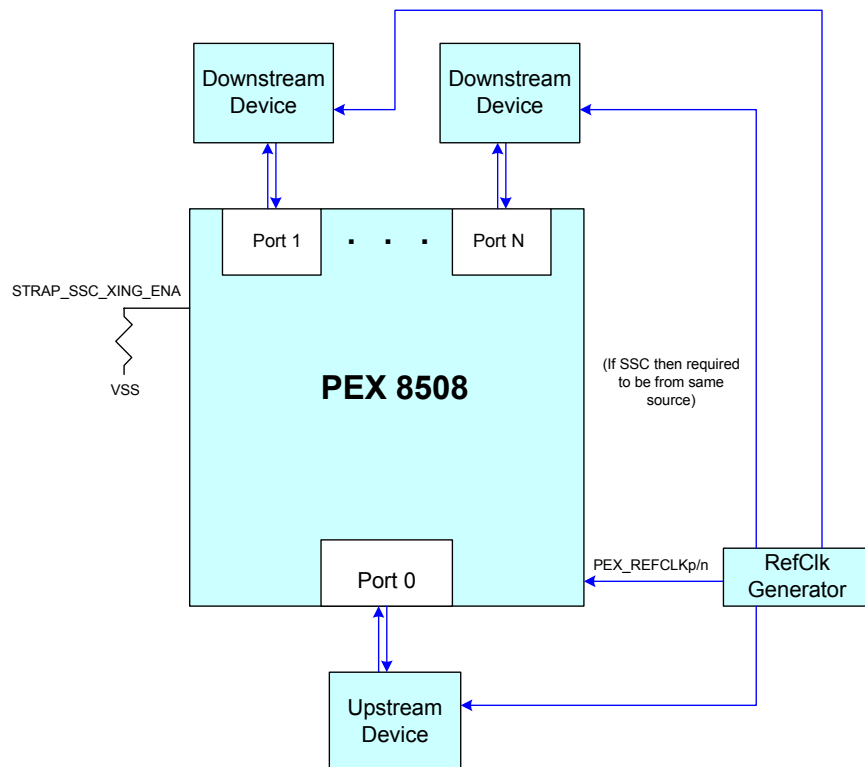

**Figure 4. Single reference clock scheme (STRAP\_SSC\_XING\_ENA pulled low)**

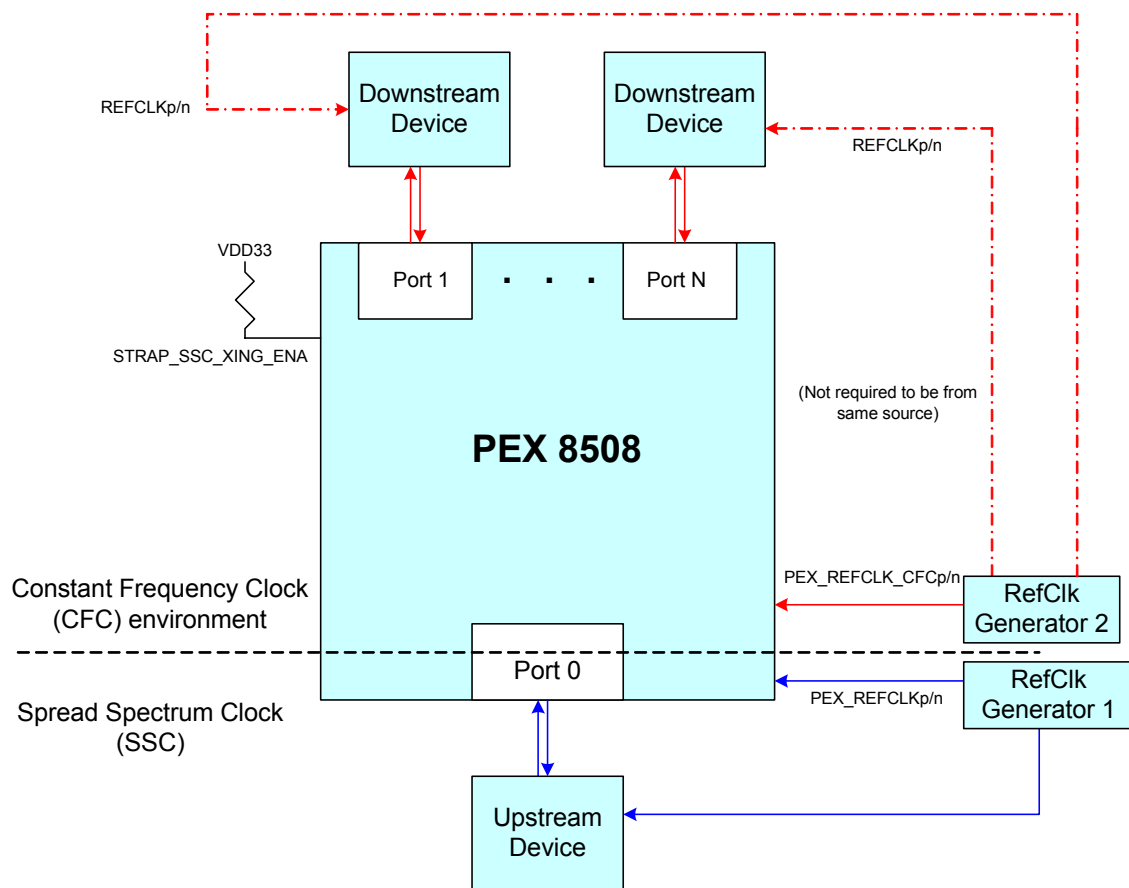


Figure 5. Dual reference clock, SSC crossing scheme (STRAP\_SSC\_XING\_ENA pulled high)

## 4. Reset Circuitry


PEX\_PERST# serves as a fundamental reset (cold and warm) to the PEX 8508. This signal is typically generated using a power-on reset circuit. The circuit can optionally have a manual reset capability to generate a “warm” reset. Typical PCI Express applications, which provide a system generated PERST#, keep the signal asserted for at least 100 ms after the board’s power is stable. PEX\_PERST# does not contain internal debounce circuitry; therefore, the system designer should guarantee that the signal has a smooth monotonic edge while being asserted or de-asserted.

## 5. EEPROM Interface

The PEX 8508 have embedded SPI EEPROM controller, which can work with devices such as the Atmel AT25256A and AT25128A EEPROM. When the PEX 8508 is operating in either transparent mode or non-transparent mode without the need for Expansion ROM, 16Kbytes of EEPROM storage is sufficient. If the application requires Expansion ROM space, a 64Kbyte EEPROM can be used with additional circuitry requirements. The lower 32Kbytes will be used for PEX 8508 register storage, while the upper 32Kbytes can be Expansion ROM storage.


The PEX 8508 implements a SPI EEPROM interface (16-bit address), which provides a direct interface to the AT25256A and AT25128A devices. This interface provides 7.8MHz serial clock (EESK), chip select (EECS#), and data input (EEDI) for the EEPROM and receives data output (EEDO) from the EEPROM. The PEX 8508 have weak internal pull-up resistors on the EEDI, EECS# and EEDO signals

to keep the EEPROM inputs/outputs from floating when not being actively driven. The system designer may choose to add stronger pull-ups (3 k $\Omega$ -10 k $\Omega$ ) on these lines.

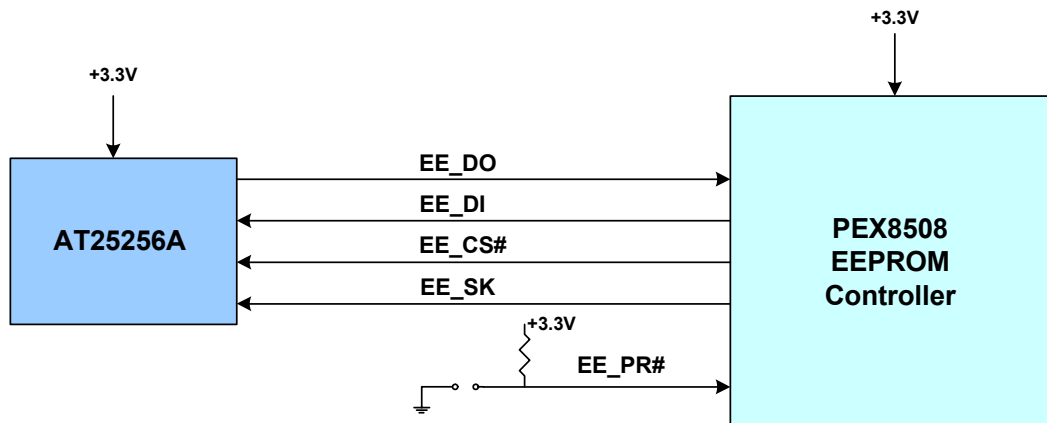

**Figure 6. PEX 8508 32-Kbyte SPI EEPROM Interface**

Applications requiring Expansion ROM may use the AT25HP512 (64Kbyte) device. This interface requires some external buffering between the PEX 8508 EEPROM controller and the AT25HP512. In order for this device to run at 7.8MHz, a 5V supply is required for the EEPROM. Level translation buffers should be used to convert the PEX 8508 3.3V output levels to 5V input levels compatible with the EEPROM. Similarly, the EEPROM's output should be level translated from 5V to 3.3V in order to prevent electrical damage to the PEX 8508 EE\_DO input. On Semiconductor's MC74VHC1GT125 tri-state buffer provides the necessary level translation for both directions. Four of these devices are required (one per pin).

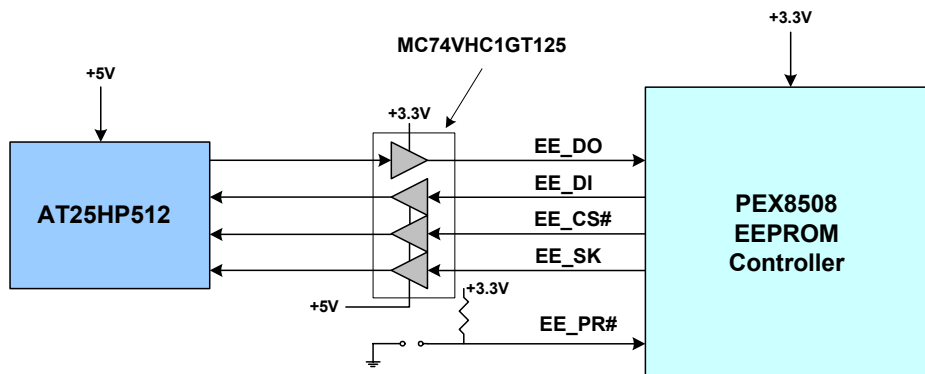


**Figure 7. PEX 8508 64-Kbyte SPI EEPROM Interface**

## 6. I2C Interface

The PEX 8508 provides an I2C compatible slave interface. This interface provides an out-of-band method for reading and writing device registers. The I2C interface is implemented as a 2-wire interface providing clock and data, and 3-pins to select the lower 3-bits of the 7-bit slave address. The upper 4-bit portion of the PEX8508's I2C address contains a fixed value of 4'b1110, therefore the 7-bit address can range in values from 70h – 77h. The 3-pin address bus can be connected to VDD33 via pull-up resistor, tied to ground, or connected to a switch that allows the system designer to change the address.

The PEX8508's I2C interface must be connected to a supply voltage of 3.3V. According to the I2C specification, the minimum pull-up resistor value for Standard-mode and Fast-mode is limited by the supply voltage. For example, if the supply voltage is 3.3V and there are no series resistors the value of  $R_{min}$  is  $966\Omega$  ( $V_{supply} - V_{ol\_max}/I_{ol\_min}$ ). The maximum value of the pull-up resistor is dependant on the bus capacitance and rise times. For example, if a Fast-mode I2C bus has 50pF of capacitance and no series resistors, the maximum pull-up resistor value will be 6.75k $\Omega$ . Please see the I2C specification for more details. [http://www.semiconductors.philips.com/products/interface\\_control/i2c/index.html](http://www.semiconductors.philips.com/products/interface_control/i2c/index.html)

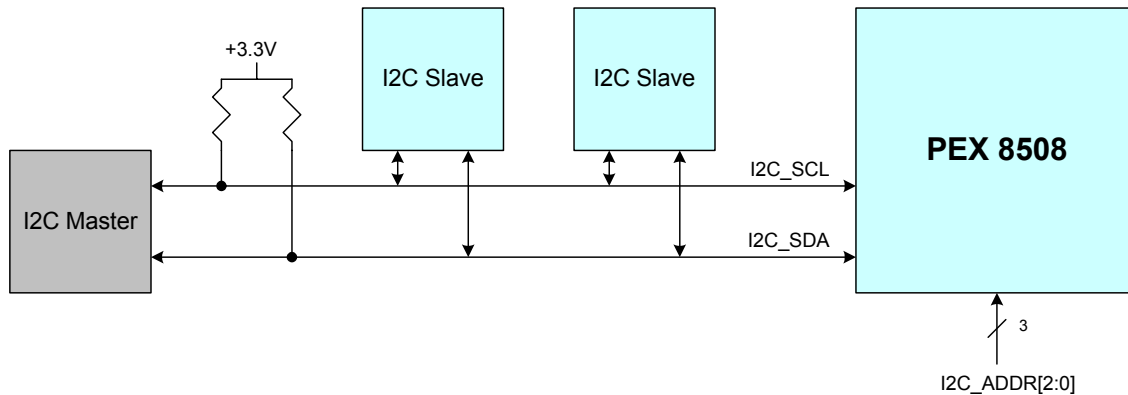


**Figure 8. I2C bus connectivity**

## 7. Hot Plug Circuitry

The PEX 8508 have the capability to be a PCI Express Hot Plug master on any of the downstream ports. Each port has nine Hot Plug pins to control various functions relating to Hot Plug. The PEX 8508 provides the following Hot Plug signals per port:

- HP\_PWREN[n]#
- HP\_PWRFLT[n]#
- HP\_ATNLED[n]#
- HP\_PWRLED[n]#
- HP\_MRL[n]#
- HP\_PRSNT[n]#
- HP\_CLKEN[n]#
- HP\_PERST[n]#
- HP\_BUTTON[n]#

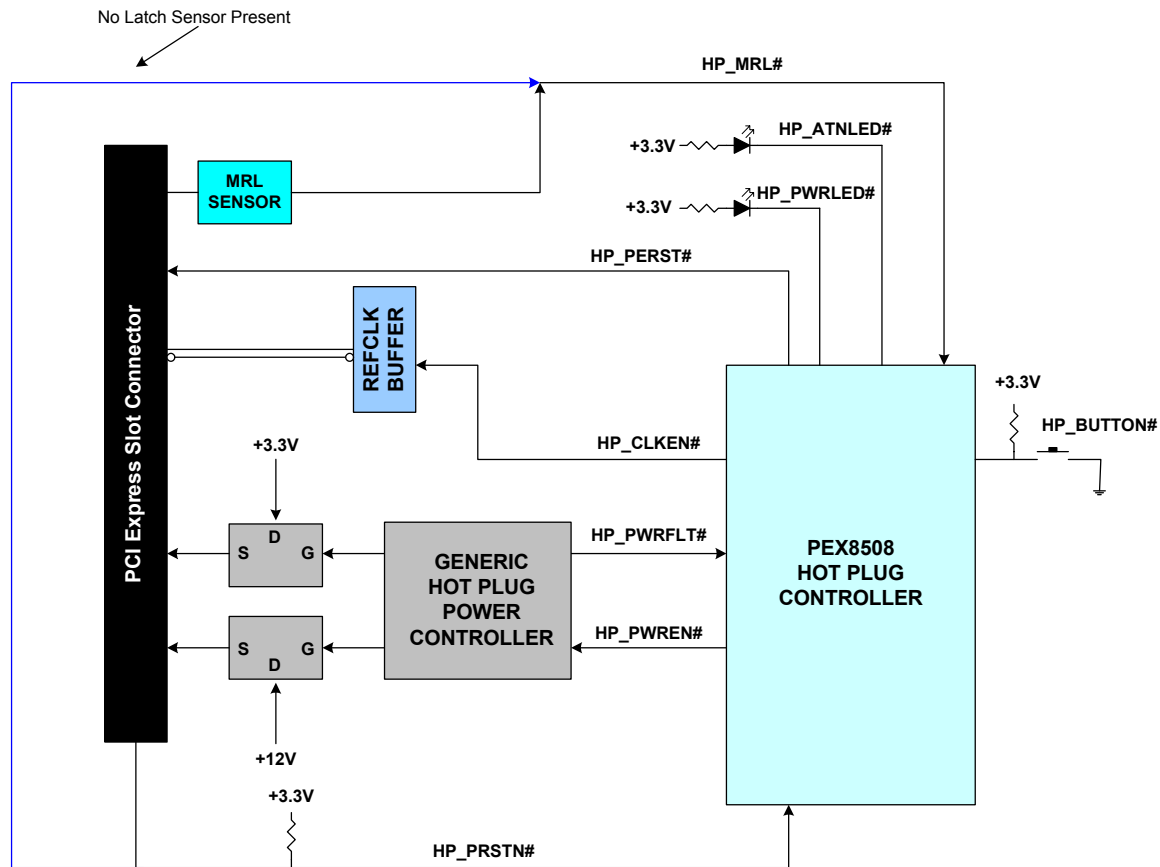

**Figure 9. PEX 8508 Hot Plug Controller Interface**

The PEX 8508 Hot Plug controller inputs have internal pull-up resistors on-chip; therefore, unused Hot Plug pins can either be left unconnected or connected the VDD33 via 3kohm-10kohm resistors. Numerous vendors such as Intersil Corporation, Texas Instruments, and Micrel Semiconductor provide PCI Express Hot Plug power controller solutions that can easily interface to the PEX 8508 Hot Plug controller.


## 8. D3-cold Power Management Support (L2 link state)

The PEX8508 supports full power management, including support for D3 cold (L2 link state). From a system design perspective, there are three elements to consider when implementing PEX8508 support for D3 cold; auxiliary power, WAKE#, and Beacon.

Prior to the removal of main power and reference clock, software must perform the necessary protocol to place the PEX8508 into the L2/L3 Ready state. The system is expected to assert PERST# prior to removing reference clock and shutting off main power. The PEX8508 has three supply rails that must remain powered in the L2 link state; VDD10X, VDD33X and VTT\_PEX. For add-in card designs, while main power is shut off, all three supplies should be powered from the card-edge connector's +3.3Vaux supply pin. The VDD10X and VDD33X supplies utilize very little power in all links states (L0, L0s, L1 and L2), and hence can be permanently powered by the +3.3Vaux supply rail.

The VTT\_PEX supply provides a termination voltage for the PCI Express transmitters and therefore utilizes much more power in the L0 state compared to the L2 state. A system designer might consider using a smart-OR power switch such as the California Micro Devices CMPWR025, to switch VTT\_PEX power when main power is shut down. All three supplies may be implemented in the same manner.

The PEX8508 supports link wakeup by either WAKE# assertion or beacon propagation. The PEX8508 will generate a beacon signal from lane 0 of its upstream port when either the WAKE# input is asserted or a beacon signal is received on any lane of a downstream port. For the former case, beacon is generated only while the WAKE# input remains asserted, hence the signal is not latched internally.

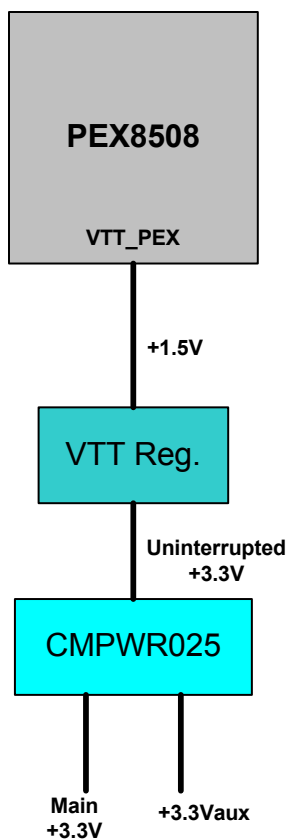

**Figure 10. Supplying VTT\_PEX during D3-cold**

## 9. Power Supplies, Power Decoupling, and Power Sequencing

### 9.1. Power Supplies

The PEX 8508 have the following power pin groups:

- VDD10– Digital core logic supply
- VDD10S – SerDes digital supply
- VDD10A – SerDes analog supply used for PLLs, biasing circuitry, and PEX\_REFCLK input buffer
- VDD10X – Core and SerDes auxiliary power supply
- VDD33 – Hot Plug/EEPROM/JTAG/Lane indicator I/O buffers
- VDD33A – PEX\_REFCLK PLL supply
- VDD33X – Auxiliary I/O power supply
- VTT\_PEX – SerDes Transmitter termination supply

At the board level, VDD10 and VDD10S can share a common 1.0V power plane. The current demands for these supplies are relatively high, so make sure that the power plane is large enough to support the specified operating current. For best performance, the 1.0V plane should have an adjacent ground plane, which will provide an interplane capacitor to supply high frequency transient currents. Provide a sufficient number of discrete capacitors for mid and low frequency decoupling. Ceramic capacitors ranging anywhere from 0.001  $\mu$ F to 0.1  $\mu$ F, and multilayer ceramic capacitors (MLCC) ranging from 10-22  $\mu$ F should be used for this supply rail.

VDD10A has a lower noise tolerance than the digital supplies, and therefore may require additional filtering depending on the 1.0V power plane noise. For frequency components less than 600 KHz, the VDD10A can tolerate noise levels up to 100 mVp-p. Between the frequency range 600 KHz – 320 MHz, the noise level must be less than 50 mVp-p. For frequency components above 320 MHz, the VDD10A can tolerate noise up to 100 mVp-p. Make sure that VDD10A power pins do not share vias with other 1.0V power pins going to the power plane.

VDD10X is used to power circuitry within the core and SerDes that are used during normal operation and when the PEX 8508 is in the D3cold state. If the PEX 8508 is not used in the D3cold state, then this supply rail can be connected directly to the main 1.0V power plane. If the PEX 8508 will enter the D3cold state, then this supply should be implemented as either a wide trace (>20-mil) or a small power island. Use at least one 10uF ceramic capacitor and a small number of 0.1uF ceramic capacitors. This supply should be relatively clean as it powers internal VCOs used to generate the beacon signal.

VDD33 power is used for signal-ended I/O buffers, such as EEPROM, JTAG, and Hot Plug pins. Although power consumption for this supply is relatively small, the output drivers have fast edge rates and therefore, require that the system designer provide adequate power decoupling to supply transient current to the drivers. It is preferred that VDD33 be implemented as a small plane, either on a signal layer or on a main power plane layer. Provide 0.1uF and/or 0.01uF ceramic capacitors, along with one or more 10uF ceramic capacitors to decouple the VDD33 power pins. The number of capacitors required depends on the number of 3.3V I/O pins utilized in the design and the existence or absence of an interplane capacitance for the VDD33 rail.

VDD33A (and VSSA\_PLL) is used to power the internal reference clock PLL. This pin may require additional filtering circuitry if the VDD33 plane has significant noise. The VDD33A supply can tolerate ripple from -100 mV to +100 mV, for frequencies above 10MHz. If additional filtering circuitry is deemed necessary, a wide trace (0.010"-0.015") can be used to power this supply pin. Use a 0  $\Omega$  resistor (0603



or 0805) in series with the main VDD33 supply, along with one or more 0.1  $\mu\text{F}$  and/or 0.01  $\mu\text{F}$  capacitors after the resistor, close to the pin. If the VDD33 rail couples significant noise into the VDD33A supply, the resistor can be exchanged for a ferrite bead to attempt to filter additional supply noise. Note that placing ferrites in a power supply path, is not a preferred method of filtering noise for supply rails. Power supplies isolated using ferrite beads, typically have limited access to interplane capacitance, which may have adverse effects on a given supply rail. In designs where VDD33A ties directly to the VDD33 power plane, make sure that VDD33A has its own dedicated via to the plane. Similarly, allow VSSA\_PLL to have its own dedicated via to the main ground plane.


The VDD33X supply is only used to power the I/O buffers for the PEX\_PERST# and WAKE# signals. If the PEX 8508 is to be placed in the D3cold state, the this supply can be implemented as a wide trace ( $> 10\text{-mil}$ ). The switching characteristics of these signals are minimal, so one 0.1 $\mu\text{F}$  capacitor should be sufficient. If the PEX 8508 will not be placed in the D3cold state, then simply connect this pin to the main VDD33 supply rail.

VTT\_PEX pins are used to set the SerDes transmitter pair's common mode voltage, and limit the output swing. Since the transmitter is implemented as a differential pair, the transient current demands required to be sourced by decoupling capacitors is minimal. Additionally, the supply rail will be less susceptible to noise if the pair is properly length matched. This supply may be implemented as a small plane. Provide at least one 10 $\mu\text{F}$  ceramic capacitor, and a sufficient number of 0.1  $\mu\text{F}$  and 0.01  $\mu\text{F}$  discrete capacitors for this supply rail. VTT\_PEX pins must remained powered while the PEX 8508 is in the D3cold state.

## 9.2. Board Level Decoupling

Board-level decoupling requirements for high-speed digital designs are highly dependant on a number of different factors such as: the printed circuit board (PCB) stack-up, differential vs. signal-ended I/O signaling, driver edge rates, number of I/Os utilized, and numerous other factors. For this reason, it is not possible to present a generalized decoupling solution that will work for all designs.

Board level power supply decoupling exists primarily in two forms. The first form of decoupling is the use of discrete capacitors, and the other form is parallel plane capacitance. Parallel plane capacitance exists between a PCBs DC power and ground planes. PCB reference planes have very little series inductance; therefore, their effective frequency range is much higher than that of discrete capacitors. Low valued discrete capacitors can typically be effective for frequencies up to 250 MHz. For frequency components higher than 250 MHz, plane capacitance provides the only effective means for decoupling. Figure 8 shows the results of measuring power plane impedance versus frequency for a PCI Express Emulation board. The plot shows the bare board power to ground impedance (shown in black) compared with the impedance of various power planes after decoupling capacitors were populated. Notice that as frequencies surpass 200 MHz the impedance profile is only affected by the bare board capacitance. Having a power and ground plane separation of 0.010" will result in approximately 100 pF/in<sup>2</sup>, while a separation of 0.004" will provide approximately 200 pF/in<sup>2</sup>. Plane capacitors provide other important benefits such as a low impedance path for AC return currents in cases where a given reference plane has a discontinuity.

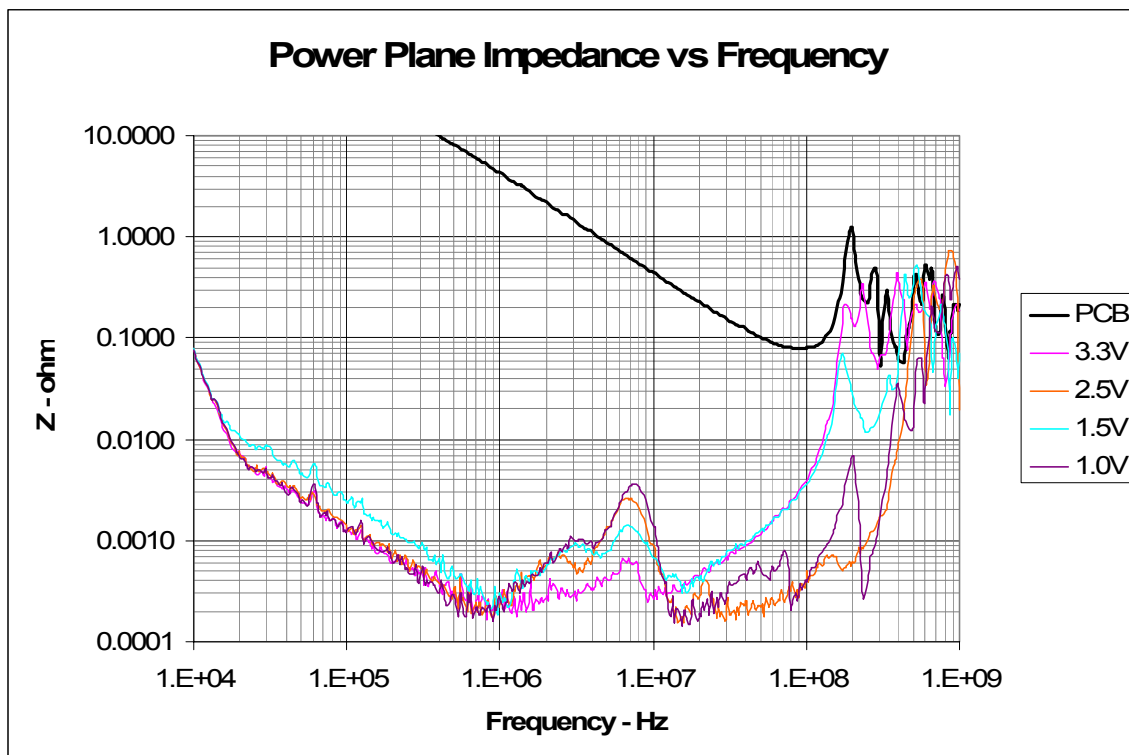

**Figure 11. Power Plane impedance vs. frequency**

As for discrete capacitors, the footprint and physical size of discrete capacitors has a significant effect on the frequencies where the capacitors provide effective decoupling. In order to minimize series inductance, smaller packaged ceramic capacitors (i.e. 0402 or 0603) should be used for mid-ranged frequency decoupling (20 MHz – 250 MHz). Use a mixed selection of capacitor values, such as 0.1  $\mu$ F and 0.01  $\mu$ F, in order to try to lower the impedance across a wide frequency range.

The physical layout of these capacitor footprints is important in determining the frequencies where they are effective. Avoid adding trace segments from the capacitor pads to the vias. These segments will add more series inductance, thereby lowering the LC resonant frequency of the discrete capacitor. Place the vias tangentially to the capacitor pads, and if possible, add multiple vias per pad (refer to “Right the First Time: A Practical Handbook on High Speed PCB and System Design” by Lee Ritchie). If a plane capacitor is used, then the placement of small discrete capacitors is not critical. Place the capacitors on the solder side of the board, underneath the BGA footprint (in the solder ball void area), and directly outside the BGA matrix. If a plane capacitor is not possible (this is typically the case for 4 and 6 layer boards), then place the capacitors as close to the pins as possible. If a PCB stackup is such that plane capacitors are not possible, the layout designer can add power or ground fill areas on signal layers. If a signal layer is referencing a DC ground plane, then fill with power, or if a signal layer is referencing a DC power plane, fill with ground. These copper fill areas tie to the main power and ground planes through component pins.

Multilayer ceramic chip capacitors (ex/ 10  $\mu$ F – 22  $\mu$ F) should be used for bulk decoupling of lower frequency components. The proximity of these capacitors is not critical; therefore, they can be placed outside the BGA matrix.

### 9.3. Power Sequencing

The PEX 8508 require three different voltage sources; 3.3V for I/O power and clock PLL power, 1.0V - 1.8V for SerDes transmitter common mode biasing, and 1.0V for SerDes/core power. VDD10, VDD10S, and VDD10A should power up first, and power down last. If sequenced properly, all supply rails should power up within 50 ms of each other.

## 10. PEX 8508 Miscellaneous Signal Groups

### 10.1. Configuration Strapping Pins

The PEX 8508 provide a number of configuration strapping signals that allow the system designer to configure various operating modes of the switch through a hardware-only mechanism. The system designer must use external pull up resistors (value between 3 k $\Omega$  – 10 k $\Omega$ ) on these lines.

Some PEX 8508 strap signals are for PLX factory use only; therefore, customers should provide a means to disable the pin functionality (pull up to VDD33). Factory use only strap signals can be pulled to VDD33 using bussed or isolated resistor networks to save board real estate.

The following PEX 8508 strapping signals are available for customer use:

- STRAP\_MODE\_SEL[1:0] – Pull up to VDD33 or pull down to VSS depending on the desired configuration. See Data Book for details.
- STRAP\_UPSTRM\_PORT\_SEL[3:0] – Pull up to VDD33 or pull down to VSS depending on the desired configuration. See Data Book for details.
- STRAP\_PORTCFG[4:0] – Pull up to VDD33 or pull down to VSS depending on the desired configuration. See Data Book for details.
- STRAP\_NT\_UPSTRM\_PORT\_SEL[3:0] – Pull up to VDD33 or pull down to VSS depending on the desired configuration. See Data Book for details.
- STRAP\_SSC\_XING\_ENA - Pull up to VDD33 or pull down to VSS depending on the desired configuration. See Data Book for details.

The following PEX 8508 signals are PLX factory use strapping signals:

- STRAP\_FACTORY\_TEST[2:1]# - Factory use only. Pull up to VDD33.
- STRAP\_TEST\_MODE[3:0] - Factory use only. Pull up to VDD33.

### 10.2. PCI Express Lane Good Indicators

PEX 8508 provides a PEX\_LANE\_GOOD[n]# indicator signal for each PCI Express lane on the device. These signal groups can be used to drive discrete LEDs, thereby giving a visual indicator that a given port's link is up and which lanes are active within the link. For example, assume port 0 is configured as an x4 PCI Express link, and the device at the other end of the link is x1. Once link training completes, the link between the two devices will be x1. PEX\_LANE\_GOOD[0]# will assert indicating that the lowest lane is active and the link between the two devices is up, while PEX\_LANE\_GOOD[3:1]# will remain de-asserted indicating that the upper three lanes have been negotiated out of the link. These output buffers can sink up to 8mA; therefore the system designer should either use low current LEDs or size the series resistor to current limit the circuit.


If the design is extremely cost sensitive and/or real estate constrained, the PEX\_LANE\_GOOD# signals can be brought out the test point vias. The system designer can probe these signals with an oscilloscope to determine if the link is up. At a minimum, a system designer should bring out lane 0 of each utilized port to a test point via. This will provide an indication that a link has at least trained as a x1.

### 10.3. JTAG Interface Signals

The PEX 8508 support a five pin JTAG Boundary scan interface. The JTAG interface consists of the following signals:

- JTAG\_TCK
- JTAG\_TMS
- JTAG\_TDI
- JTAG\_TDO
- JTAG\_TRST#

At the board level, JTAG\_TDI, JTAG\_TMS, and JTAG\_TCK should be pulled up to VDD33 with 1 k $\Omega$ -5 k $\Omega$  resistors, while JTAG\_TRST# should be pulled down to VSS with a 1 k $\Omega$ -5 k $\Omega$  resistor. A 33  $\Omega$  series terminator can be added to JTAG\_TDO to improve signal quality. Figure 8 shows a generic JTAG interconnection.

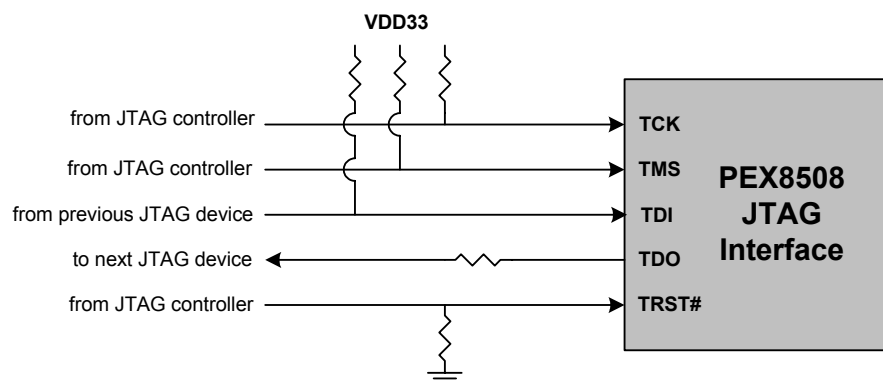

**Figure 12. Generic JTAG interface**